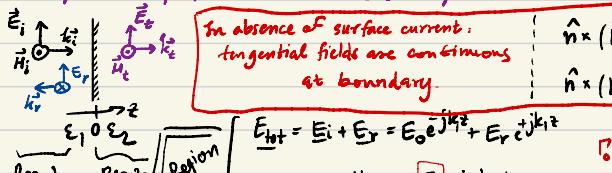


Reflection & Transmission

Consider plane wave perpendicular incidence onto plane boundaries



In absence of surface current:
tangential fields are continuous
at boundary.

$$\begin{aligned} \vec{E}_{\text{tot}} &= \vec{E}_i + \vec{E}_r = E_0 e^{jk_1 z} + E_r e^{jk_2 z} \\ &= E_0 e^{jk_1 z} \left(1 + \frac{E_r}{E_0} e^{jk_2 z} \right) \end{aligned}$$

$$\begin{aligned} \vec{H}_{\text{tot}} &= \vec{H}_i + \vec{H}_r = H_0 e^{-jk_1 z} + H_r e^{-jk_2 z} \\ &= \frac{E_0}{\eta_1} e^{-jk_1 z} - \frac{E_r}{\eta_2} e^{-jk_2 z} \\ &= \frac{E_0}{\eta_1} e^{-jk_1 z} \left(1 - \frac{E_r}{E_0} e^{jk_2 z} \right) \end{aligned}$$

$$\hat{n} \times (\vec{E}_i - \vec{E}_r) = 0$$

$$\hat{n} \times (\vec{H}_i - \vec{H}_r) = \vec{J}_s = 0$$

Due to continuity of tangential fields

$$E_{\text{tot}}^2|_{z=0} = E_{\text{tot}}^2|_{z=0}$$

$$H_{\text{tot}}^2|_{z=0} = H_{\text{tot}}^2|_{z=0}$$

$$\frac{E_{\text{tot}}^2}{H_{\text{tot}}^2}|_{z=0} = \frac{E_{\text{tot}}^2}{H_{\text{tot}}^2}|_{z=0}$$

"wave impedance" ≠ "intrinsic impedance"

1D Transmission line

Example of lumped element

• Coaxial cable



• Stripline



Idealization


- (1) Structure is uniform and "small" in two directions (compared to wavelength)
but extending in other direction
⇒ lumped approx. good for two directions
not third (propagation dir.)

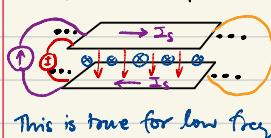- (2) The structure has two distinct conductors



(note that not considering
rectangular / circular waveguide yet)
↳ Pozar ch.3


Jan 27, 2025 A parallel plate transmission




This is true for low freq

Assume \vec{E} & \vec{H} has no \hat{z} component, i.e. $E_z = 0, H_z = 0 \Rightarrow$ TEM mode

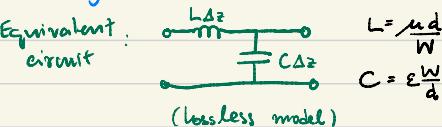Discretize this into pieces with a size way smaller than λ . ($\Delta z \ll \lambda$)



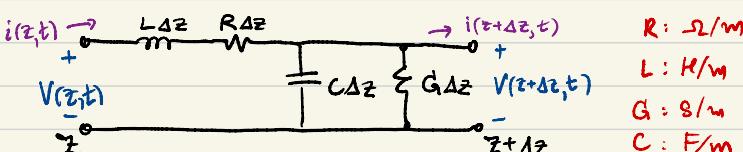If resistive loss (R) and dielectric loss are considered:



KVL:

$$V(z,t) - L \Delta z \frac{d}{dt} i(z,t) - R \Delta z i(z,t) - V(z+\Delta z, t) = 0$$

$$\frac{V(z,t) - V(z+\Delta z, t)}{\Delta z} = L \frac{d}{dt} i(z,t) + R i(z,t)$$

$$\Delta z \rightarrow 0: \left[-\frac{\partial}{\partial z} V(z,t) = L \frac{d}{dt} i(z,t) + R i(z,t) \right] \quad (1)$$

KCL: $i(z,t) - i(z+\Delta z, t) - C \Delta z \frac{d}{dt} V(z+\Delta z, t) - G \Delta z V(z+\Delta z, t) = 0$

$$\frac{i(z,t) - i(z+\Delta z, t)}{\Delta z} = C \frac{d}{dt} V(z+\Delta z, t) + G V(z+\Delta z, t)$$

$$\Delta z \rightarrow 0: \left[-\frac{\partial}{\partial z} i(z,t) = C \frac{d}{dt} V(z,t) + G V(z,t) \right] \quad (2)$$

(1), (2) \Rightarrow Telegrapher's equation:

$$\text{For sinusoid time-dependent } V(z,t) = \operatorname{Re}[V(z)e^{j\omega t}]$$

$$I(z,t) = \operatorname{Re}[I(z)e^{j\omega t}]$$

$$(1) \Rightarrow -\frac{d}{dz}V(z) = j\omega L I(z) + R I(z)$$

$$-\frac{d}{dz}V(z) = (j\omega L + R) I(z) \Rightarrow I(z) = -\frac{1}{(j\omega L + R)} \frac{d}{dz}V(z) \quad \left. \begin{array}{l} \frac{1}{(j\omega L + R)} \cdot \frac{d^2}{dz^2}V(z) = (j\omega C + G) V(z) \\ \downarrow \end{array} \right.$$

$$(2) \Rightarrow -\frac{d}{dz}I(z) = (j\omega C + G)V(z)$$

Solve wave eqs:

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

$$I(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z}$$

$$\Rightarrow I(z) = -\frac{1}{R+j\omega L} \frac{dV(z)}{dz} = -\frac{1}{R+j\omega L} (-\gamma V_0^+ e^{-\gamma z} + \gamma V_0^- e^{\gamma z}) \\ = \frac{1}{R+j\omega L} \{ \gamma V_0^+ e^{-\gamma z} - \gamma V_0^- e^{\gamma z} \}$$

$$I(z) = \frac{\sqrt{R+j\omega L}}{\sqrt{G+j\omega C}} (V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z})$$

$1/z_0$

Characteristic impedance:

and

$$\frac{d^2}{dt^2}V(z) - \gamma^2 V(z) = 0$$

$$\frac{d^2}{dt^2}I(z) - \gamma^2 I(z) = 0$$

Helmholtz
eqs.

$$\text{where } \gamma = \alpha + j\beta = \sqrt{(R+j\omega L)(G+j\omega C)}$$

(complex propagation constant)

depends on propagation direction

$$\lambda = \frac{2\pi}{\beta}$$

$$v_p = \frac{\omega}{\beta}$$

\Rightarrow Lossless line: $R=0, G=0 \Rightarrow \gamma = \alpha + j\beta = j\omega\sqrt{LC}$

$$\Rightarrow \alpha = 0 \text{ & } \beta = \omega\sqrt{LC}, Z_0 = \sqrt{L/C}$$

$$\boxed{V(z) = V_0^+ e^{-j\beta z} + V_0^- e^{+j\beta z}}$$


$$\boxed{I(z) = \frac{V_0^+ e^{-j\beta z} - V_0^- e^{+j\beta z}}{Z_0}}$$

$$\gamma = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{LC}}$$

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$$


Comments on transmission line (T-line) propagation

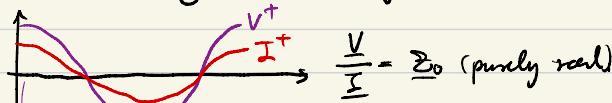(1) Current and voltage are traveling waves



V and I on T-line follow same sign convention

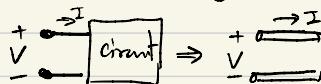as circuit theory \Rightarrow current is "positive", flows into "+" terminal



(2) Lossless line: Real Z_0 \Rightarrow only means V and I in phase.

No power dissipation

Field Analysis of transmission \Rightarrow Pozar Ch.3

\rightarrow microstrip (Pozar ch.3)

$\frac{d}{d\zeta} \frac{V(z)}{I(z)}$ The substrate is electrically thin ($d \ll \lambda$),

$-E$ so the fields are quasi-TEM

$-H$

• propagation constant $\beta = k_0 \sqrt{\epsilon_r}$


• phase velocity: $v_p = \frac{c}{\sqrt{\epsilon_r}}$ effective dielectric constant

Jan 29

* Reflection: In general, along T-line we have both +z, -z-waves: +z incident wave, -z reflected wave

traveling waves superposition \rightarrow standing wave

Transmission line discontinuity

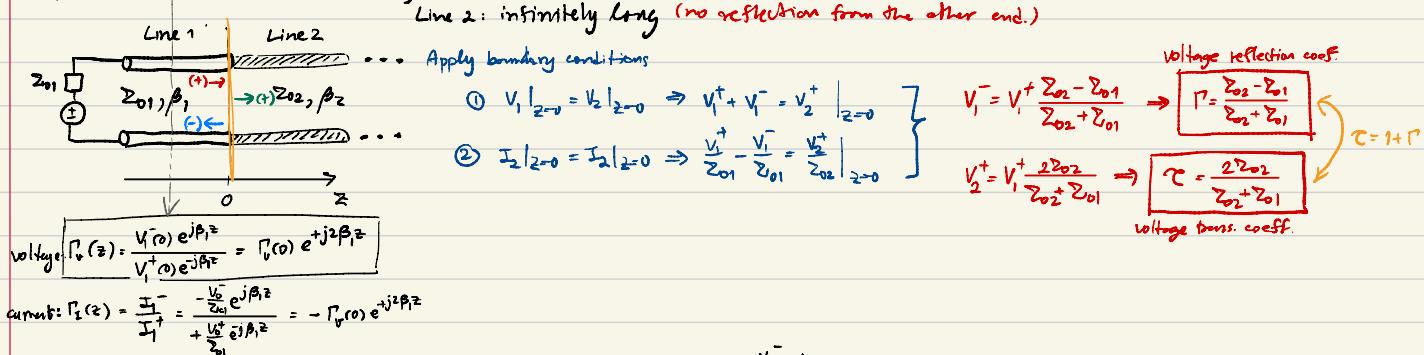

• Wave impedance

$$\Sigma(z) = \frac{V(z)}{I(z)} = \frac{V_1^+ + V_1^-}{I_1^+ + I_1^-} = \frac{V_1^+ e^{j\beta_1 z} + V_1^- e^{-j\beta_1 z}}{\frac{V_0}{Z_{01}} e^{j\beta_1 z} - \frac{V_0}{Z_{01}} e^{-j\beta_1 z}} = Z_0 \frac{1 + \frac{V_0}{Z_{01}} e^{j2\beta_1 z}}{1 - \frac{V_0}{Z_{01}} e^{j2\beta_1 z}}$$

$$\Gamma_v(z) = \frac{\Sigma(z) - Z_0}{\Sigma(z) + Z_0}$$

$$\Gamma = \frac{V^-}{V^+} = \Gamma_v^0 e^{j2\beta_1 z}|_{z=0}$$

• Loaded line

$$\text{At } z=0, \Sigma(0) = \Sigma_L$$

$$\Gamma_0 = \frac{\Sigma_L - Z_0}{\Sigma_L + Z_0}$$

$$\Sigma(m) = \Sigma_L = Z_0 \frac{1 + \Gamma_0}{1 - \Gamma_0}$$

$$\Sigma(-d) = Z_0 \frac{1 + \Gamma_0(-d)}{1 - \Gamma_0(-d)} = Z_0 \frac{1 + \Gamma_0 e^{-j2\beta d}}{1 - \Gamma_0 e^{-j2\beta d}}$$

$$\begin{aligned} \Sigma(-d) &= \Sigma_0 \frac{(\Sigma_0 + Z_0) e^{j\beta d} + (\Sigma_0 - Z_0) e^{-j\beta d}}{(\Sigma_0 + Z_0) e^{j\beta d} - (\Sigma_0 - Z_0) e^{-j\beta d}} \\ &= \Sigma_0 \frac{\Sigma_0 \cos \beta d + j \Sigma_0 \sin \beta d}{\Sigma_0 \cos \beta d - j \Sigma_0 \sin \beta d} \end{aligned}$$

$$\Rightarrow \Sigma(-d) = \Sigma_0 \frac{\Sigma_0 + j 2 \tan \beta d}{\Sigma_0 - j 2 \tan \beta d}$$


★ Examples

$$\textcircled{1} \text{ Matched line: } \Sigma_L = \Sigma_0 : \Gamma_0 = \frac{\Sigma_0 - Z_0}{\Sigma_0 + Z_0} = 0 ; \Sigma(d) = \Sigma_0$$

$$\textcircled{2} \text{ Shorted line: } \Sigma_L = 0 : \Gamma_0 = -1 ; \Sigma(d) = \Sigma_0 j \tan \beta d$$

$$\textcircled{3} \text{ Open line: } \Sigma_L = \infty : \Gamma_0 = 1 ; \Sigma(d) = \frac{\Sigma_0}{j \cot \beta d} = \Sigma_0 (-j \cot \beta d)$$
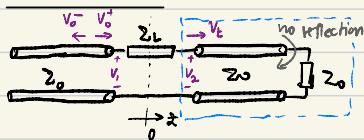
$$\textcircled{4} \text{ } d = \frac{\pi}{4} \Rightarrow \beta d = \frac{(2\pi)}{\lambda} \left(\frac{\pi}{4} \right) = \frac{\pi}{2} \Rightarrow \Sigma(d) = \frac{\Sigma_0^2}{Z_0} \text{ Quarter-wave transformer.}$$



$$V_1 = V_0^+ + V_1^- = V_0^+ (1 + \Gamma)$$

$$V_2 = V_L \text{ (no reflection)}$$

$$I_1 = I_0^+ + I_0^- = \frac{V_0^+ - V_0^-}{Z_0} = \frac{V_0^+}{Z_0} (1 - \Gamma)$$

$$I_2 = \frac{V_L}{Z_L}$$

$$\text{KVL: } V_1 - V_2 = V_L \rightarrow V_0^+ (1 + \Gamma) - V_L = V_L$$


$$\text{KCL: } I_1 = I_2 \rightarrow \frac{V_0^+ (1 - \Gamma)}{Z_0} = \frac{V_L}{Z_L} = \frac{V_L}{Z_0}$$

$$V_0^+ (1 + \Gamma) - \frac{Z_0 V_L}{Z_0} = V_L \Rightarrow V_0^+ = \frac{(1 - \frac{Z_0}{Z_L})}{(1 + \Gamma)} V_L$$

$$\therefore \frac{1 + \Gamma}{1 - \Gamma} = 1 + \frac{Z_L}{Z_0} = 1 + \frac{Z_L}{Z_0} \text{ normalized impedance}$$

$$\rightarrow \Gamma = \frac{Z_L}{Z_0} = \frac{Z_L}{Z_0 + 2Z_0}$$

Simplified circuit.

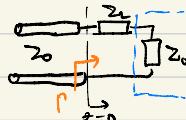

$$R = \frac{(Z_L + Z_0) - Z_0}{(Z_L + Z_0) + Z_0} = \frac{Z_L}{Z_L + 2Z_0}$$

• Reflection coefficient: Γ

• Return loss: $RL = -20 \log_{10} |\Gamma|$

• Insertion loss: $IL = -20 \log_{10} |C| , C = 1 + \Gamma$

$$0.1 \Rightarrow 20 \text{ dB}$$

$$0.01 \Rightarrow 40 \text{ dB}$$

$$0.001 \Rightarrow 60 \text{ dB}$$

