


Feb 10

Microwave Network (Pozar Ch. 4)

Solving complicated Maxwell equation at RF

→ Extending network theory at lower freq. to handle microwave network

Impedance Matrix

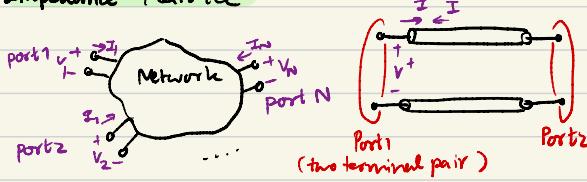

Terminal voltage and terminal current.

$$V_h = V_h^+ + V_h^-$$

$$I_h = I_h^+ - I_h^-$$

related by $N \times N$ impedance matrix

$$\begin{pmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{pmatrix} = \begin{pmatrix} Z_{11} & Z_{12} & \cdots & Z_{1N} \\ Z_{21} & Z_{22} & \cdots & Z_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Z_{N1} & Z_{N2} & \cdots & Z_{NN} \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{pmatrix} \Rightarrow [V] = [Z] [I]$$

$$Z_{ij} = \frac{V_i}{I_j} \quad I_k = 0 \text{ for } k \neq j$$


Driving port j with I_j ,
measure voltage at port i (V_i)
when other ports are open-circuited.

Example

$\frac{Z_A}{Z_C}$	$\frac{Z_B}{Z_C}$
port 1	port 2

$$[Z] = \begin{bmatrix} Z_A + Z_C & Z_C \\ Z_C & Z_B + Z_C \end{bmatrix}$$

(reciprocal network)

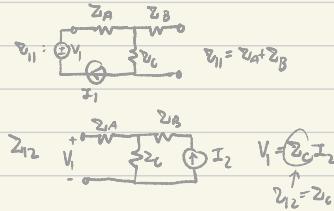
Admittance matrix: $[I] = [Y][V] \Rightarrow [Y] = [Z]^{-1}$

$$\begin{pmatrix} I_1 \\ I_2 \\ \vdots \\ I_N \end{pmatrix} = \begin{pmatrix} Y_{11} & Y_{12} & \cdots & Y_{1N} \\ Y_{21} & Y_{22} & \cdots & Y_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ Y_{N1} & Y_{N2} & \cdots & Y_{NN} \end{pmatrix} \begin{pmatrix} V_1 \\ V_2 \\ \vdots \\ V_N \end{pmatrix} \quad Y_{ij} = \frac{I_j}{V_i} \quad V_h = 0 \text{ for } h \neq i$$


Driving port j with voltage V_j
measure current I_i at port i
while short circuit other ports

Scattering matrix (Chap 4.3)

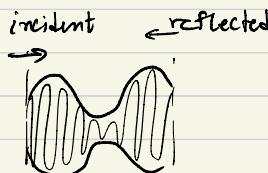
Difficult to measure voltage and current as they are likely function of position



Scattering matrix: generalization of the notion of reflection/transmission coefficient.

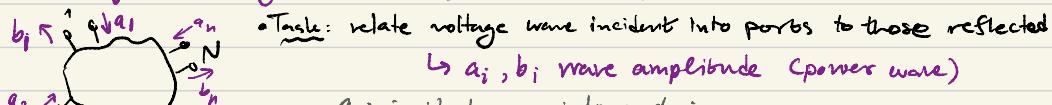 a_i : incident wave into port i b_i : reflected wave out of port j
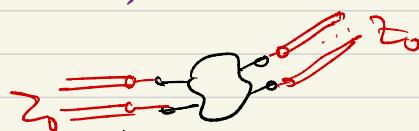
$$a_i = \frac{V_i^+}{\sqrt{Z_i}}, \quad b_i = \frac{V_i^-}{\sqrt{Z_i}}$$



Z_i is the impedance of the network looking into port i ,
which is equivalent to the Z_0 of the transmission line at port i ,
assuming infinitely long T-lines (no reflection).

Z_i, Z_j defined as normalized impedance
for port i and port j usually
(not necessarily) equal to Z_0 of the
T-line attached to the port.

Discussion


$$V_i = V_i^+ + V_i^- = a_i \sqrt{Z_i} + b_i \sqrt{Z_i} = (a_i + b_i) \sqrt{Z_i}$$

$$I_i = I_i^+ - I_i^- = \frac{V_i^+ - V_i^-}{Z_i} = (a_i - b_i) / \sqrt{Z_i}$$

$$a_i = \frac{V_i^+ + Z_i I_i}{2\sqrt{Z_i}}, \quad b_i = \frac{V_i^- - Z_i I_i}{2\sqrt{Z_i}}$$

Net power into port i

$$\begin{aligned} P_i &= \operatorname{Re}\{V_i I^*\} \\ &= \operatorname{Re}\left\{(a_i + b_i) \cdot \sqrt{2} e^{j\theta} (a_i^* - b_i^*) \frac{1}{Z_i}\right\} \\ &= \operatorname{Re}\left\{|a_i|^2 - |b_i|^2 - a_i b_i^* + (a_i b_i^*)^*\right\} \\ &\quad \text{purely imaginary} \end{aligned}$$

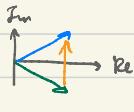

$P_i = |a_i|^2 - |b_i|^2 \rightarrow$ wave amplitude (power wave) are defined in a way that

$$|a_i|^2 = |V_i^+|^2 / Z_i : \text{incident power}$$

$$|b_i|^2 = |V_i^-|^2 / Z_i : \text{scattered power}$$

$$\vec{a} = \begin{pmatrix} a_1 \\ a_2 \\ \vdots \\ a_N \end{pmatrix}, \vec{b} = \begin{pmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{pmatrix}, P = \sum_{i=1}^N P_i = \vec{a}^\dagger \vec{a} - \vec{b}^\dagger \vec{b}$$

(dagger) denotes conjugate transpose "Hermitian" conjugate


Define scattering matrix incident and scattered wave

$$[\vec{b}] = [S][\vec{a}] : \begin{pmatrix} b_1 \\ b_2 \\ \vdots \\ b_N \end{pmatrix} = \begin{pmatrix} S_{11} & S_{12} & \cdots & S_{1N} \\ S_{21} & S_{22} & \cdots & S_{2N} \\ \vdots & \vdots & \ddots & \vdots \\ S_{N1} & S_{N2} & \cdots & S_{NN} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \\ \vdots \\ a_N \end{pmatrix}$$

output

$$S_{ij} = \frac{b_j}{a_i} \Big|_{a_k=0, k \neq i}$$


input

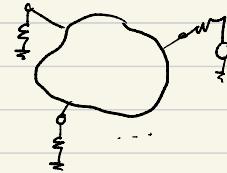

Measure the scattered wave at port i, make sure that all others are matched to

The reference impedance of S-parameters.

Example 1: evaluate S-param for 50Ω ref.

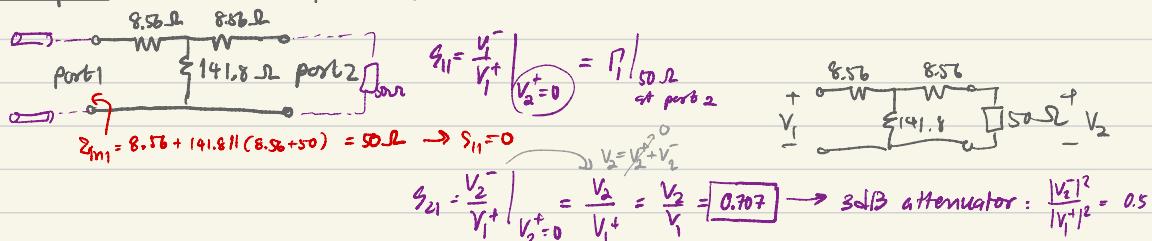

Feb 12

Example 2:

$$\begin{aligned} \text{Circuit diagram: } & \text{Port 1: } \frac{b_1}{a_1} = \frac{V_1^-}{V_1^+} \Big|_{V_2=0} = R; \quad \text{Port 2: } \frac{b_2}{a_2} = \frac{V_2^-}{V_2^+} \Big|_{V_1=0} = \frac{V_2}{V_1^+} = \frac{V_2}{V_1} (1+S_{11}) = \frac{2Z_0}{Z_0+Z_1} \cdot \left(1 + \frac{Z_1}{Z_0+Z_1}\right) = \frac{2Z_0}{2Z_0+Z_1} \\ & S_{11} = \frac{b_1}{a_1} = \frac{V_1^-}{V_1^+} \Big|_{V_2=0} = \frac{V_1^-}{V_1^+} = \frac{V_1^-}{V_1} (1+R) = \frac{V_1^-}{V_1} S_{11} \end{aligned}$$

Example 3:

$$\textcircled{1} \text{ Find } S_{11} : S_{11} = R = \frac{(2/Z_{01}) - Z_{01}}{(2/Z_{01}) - Z_{01} + Z_{02}} = \frac{\frac{2Z_{02}}{Z_{01}} - Z_{01}}{\frac{2Z_{02}}{Z_{01}} + Z_{01}} = \frac{2(Z_{01} - Z_{02}) - Z_{01}Z_{02}}{2(Z_{01} + Z_{02}) + Z_{01}Z_{02}}$$

$$\text{Automatically : } S_{22} = \frac{\Sigma (Z_{01} - Z_{02}) - Z_{01}Z_{02}}{\Sigma (Z_{01} + Z_{02}) + Z_{01}Z_{02}} \quad \frac{V_1^+}{V_1^-} \frac{V_2^+}{V_2^-} = \frac{V_1^+}{V_1^-} S_{11} = \frac{V_1^+}{V_1^-} \frac{V_2^+}{V_2^-} S_{11}$$

$$\textcircled{2} \text{ Find } S_{21} : S_{21} = \frac{V_2^- / \sqrt{Z_{02}}}{V_1^+ / \sqrt{Z_{01}}} = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot \frac{V_2^-}{V_1^+} = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot \frac{V_2}{V_1/(1+R)} = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot (1+S_{11}) = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot \left(1 + \frac{\Sigma (Z_{01} - Z_{02}) - Z_{01}Z_{02}}{\Sigma (Z_{01} + Z_{02}) + Z_{01}Z_{02}}\right)$$

$$S_{21} = \sqrt{\frac{Z_{01}}{Z_{02}}} \cdot \frac{1}{\Sigma (Z_{01} + Z_{02}) + Z_{01}Z_{02}}$$


Example 4: Section of T-line

$$\text{Circuit diagram: } \frac{b_1}{a_1} = \frac{V_1^-}{V_1^+} = \frac{V_1^+ e^{j\theta}}{V_1^+} = e^{j\theta} = S_{11}$$

$$S_{11} = 0, S_{22} = 0$$

$$[S] = \begin{pmatrix} 0 & e^{j\theta} \\ e^{j\theta} & 0 \end{pmatrix}$$

Reference plane

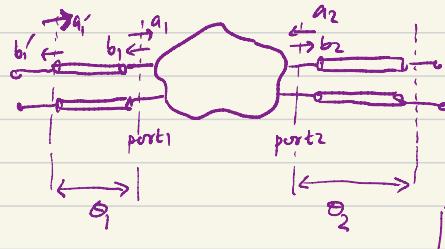

$$\begin{aligned} \begin{pmatrix} b_1 \\ b_2 \end{pmatrix} &= \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} a_1 \\ a_2 \end{pmatrix} \\ \downarrow \\ \begin{pmatrix} b'_1 \\ b'_2 \end{pmatrix} &= \begin{pmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{pmatrix} \begin{pmatrix} a'_1 \\ a'_2 \end{pmatrix} \\ \therefore [S'] &= \begin{pmatrix} e^{-j2\theta_1} S_{11} & e^{-j(\theta_1+\theta_2)} S_{12} \\ e^{j(\theta_1+\theta_2)} S_{21} & e^{-j2\theta_2} S_{22} \end{pmatrix} \end{aligned}$$

$$\begin{aligned} a_1 &= a'_1 \cdot e^{-j\theta_1} & b'_1 &= b_1 \cdot e^{-j\theta_1} \\ a_2 &= a'_2 \cdot e^{-j\theta_2} & b'_2 &= b_2 \cdot e^{-j\theta_2} \end{aligned}$$

$$\begin{aligned} \begin{pmatrix} b'_1 \\ b'_2 \end{pmatrix} &= \begin{pmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{pmatrix} \begin{pmatrix} S_{11} & S_{12} \\ S_{21} & S_{22} \end{pmatrix} \begin{pmatrix} e^{-j\theta_1} & 0 \\ 0 & e^{-j\theta_2} \end{pmatrix} \begin{pmatrix} a'_1 \\ a'_2 \end{pmatrix} \\ &= \begin{pmatrix} S'_{11} & S'_{12} \\ S'_{21} & S'_{22} \end{pmatrix} \end{aligned}$$

Properties of S-parameter

① Reciprocity: can exchange excitation & measurement power without changing relationship between them.



For reciprocity to hold: the circuit must be

- ① linear
- ② time-invariant
- ③ contains no V/I source e.g. amplifier
- ④ made of reciprocal material

• examples: transmission line filter

impedance matching antenna

reciprocal

amplifier, circulator
transistor

nontreciprocal

② Lossless network: dissipates no power, i.e., scattered powers = incident power

$[S]$ is lossless if $[S] = \text{unitary}$: $[S]^{-1} = [S^*]$

$$\sum_{k=1}^N S_{ki} S_{kj}^* = \delta_{ij} \leftarrow \text{Kronecker delta function } \delta_{ij} = \begin{cases} 1 & i=j \\ 0 & \text{otherwise} \end{cases}$$


	S	Z	Y	$ABCD$
S_{11}	S_{11}	$\frac{(Z_{11} - Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 - Y_{11})(Y_0 + Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{A + B/Z_0 - CZ_0 - D}{A + B/Z_0 + CZ_0 + D}$
S_{12}	S_{12}	$\frac{2Z_{12}Z_0}{\Delta Z}$	$\frac{-2Y_{12}Y_0}{\Delta Y}$	$\frac{2(AD - BC)}{A + B/Z_0 + CZ_0 + D}$
S_{21}	S_{21}	$\frac{2Z_{21}Z_0}{\Delta Z}$	$\frac{-2Y_{21}Y_0}{\Delta Y}$	$\frac{2}{A + B/Z_0 + CZ_0 + D}$
S_{22}	S_{22}	$\frac{(Z_{11} + Z_0)(Z_{22} - Z_0) - Z_{12}Z_{21}}{\Delta Z}$	$\frac{(Y_0 + Y_{11})(Y_0 - Y_{22}) + Y_{12}Y_{21}}{\Delta Y}$	$\frac{-A + B/Z_0 - CZ_0 + D}{A + B/Z_0 + CZ_0 + D}$
Z_{11}	Z_{11}	Z_{11}	$\frac{Y_{22}}{ Y }$	$\frac{A}{C}$
Z_{12}	Z_{12}	Z_{12}	$\frac{-Y_{12}}{ Y }$	$\frac{AD - BC}{C}$
Z_{21}	Z_{21}	Z_{21}	$\frac{-Y_{21}}{ Y }$	$\frac{1}{C}$
Z_{22}	Z_{22}	Z_{22}	$\frac{Y_{11}}{ Y }$	$\frac{D}{C}$
Y_{11}	Y_{11}	$\frac{Z_{22}}{ Z }$	Y_{11}	$\frac{D}{B}$
Y_{12}	Y_{12}	$\frac{-Z_{12}}{ Z }$	Y_{12}	$\frac{BC - AD}{B}$
Y_{21}	Y_{21}	$\frac{-Z_{21}}{ Z }$	Y_{21}	$\frac{-1}{B}$
Y_{22}	Y_{22}	$\frac{Z_{11}}{ Z }$	Y_{22}	$\frac{A}{B}$
A	$\frac{(1 + S_{11})(1 - S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{Z_{11}}{Z_{21}}$	$\frac{-Y_{22}}{Y_{21}}$	A
B	B	$\frac{Z_0 \frac{(1 + S_{11})(1 + S_{22}) - S_{12}S_{21}}{2S_{21}}}{Z_{21}}$	$\frac{-1}{Y_{21}}$	B
C	C	$\frac{1}{Z_0} \frac{(1 - S_{11})(1 - S_{22}) - S_{12}S_{21}}{2S_{21}}$	$\frac{- Y }{Y_{21}}$	C
D	D	$\frac{(1 - S_{11})(1 + S_{22}) + S_{12}S_{21}}{2S_{21}}$	$\frac{-Y_{11}}{Y_{21}}$	D

$$|Z| = Z_{11}Z_{22} - Z_{12}Z_{21}; \quad |Y| = Y_{11}Y_{22} - Y_{12}Y_{21}; \quad \Delta Y = (Y_{11} + Y_0)(Y_{22} + Y_0) - Y_{12}Y_{21}; \quad \Delta Z = (Z_{11} + Z_0)(Z_{22} + Z_0) - Z_{12}Z_{21}; \quad Y_0 = 1/Z_0.$$


Feb 17

How to handle S-parameters for complicated networks?

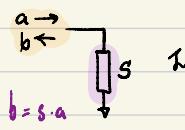⇒ Use signal flow graph as an alternative to circuit diagrams.



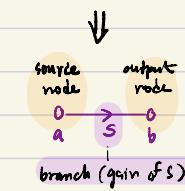(can be described by linear equation from inspecting a graph).



Remarks: 1) the arrow points from the source node to the output node.


2) A node may have multiple incoming or outgoing paths.

However, the source node of the overall SFG can only have outgoing paths.

3) The value of any variable/node is equal to the sum of nodes incoming to that node multiplied by their path gain.



Example:

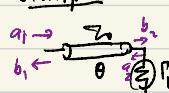

$$(-[S_{11}] - [I])$$

① Sketch all wave amplitude.

② For SFG, indicate all wave amplitudes and nodes



$$\begin{aligned} a_1 &\rightarrow b_2 \quad a_2 \\ e^{j\theta} & \quad \quad \quad e^{-j\theta} \\ a_1 &\rightarrow b_2 \quad a_2 \\ e^{j\theta} & \quad \quad \quad e^{-j\theta} \\ q_1' &= \frac{b_1}{a_1} = R_L e^{-j\theta} \\ q_2' &= \frac{b_2}{a_2} = R_L e^{j\theta} \end{aligned}$$

$$b_2 = a_1 e^{j\theta}$$

$$a_2 = R_L b_1$$

$$b_1 = a_2 e^{-j\theta}$$

Example:

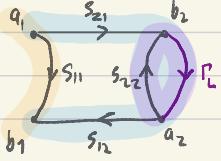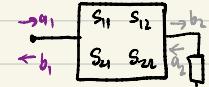

$$b_2 = S_{21}a_1 + S_{22}a_2 \quad (1)$$

$$a_2 = R_L(b_1 + S_{21}a_1) \quad (2)$$

$$a_2 = \frac{R_L S_{21}}{1 - S_{21} R_L} a_1 \quad (3)$$

$$q_1' = \frac{b_1}{a_1} = \frac{S_{11}a_1 + S_{12}a_2}{a_1} = S_{11} + S_{12} \frac{a_2}{a_1} = S_{11} + \frac{S_{12} S_{21} R_L}{1 - S_{21} R_L} a_1 \quad \text{open-loop gain}$$

1-loop gain

Decomposition Rule (Reminder: node represents wave amplitude)

$$1) \quad \begin{array}{c} S_{21} \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_{32} \\ \text{---} \\ b_2 \end{array} \quad \begin{array}{c} S_{23} \\ \text{---} \\ b_3 \end{array} \quad \equiv \quad \begin{array}{c} S_{21} S_{32} \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_{23} \\ \text{---} \\ b_3 \end{array} \quad \text{replace two series branches}$$

with common node with single branch with gain
(product of gains of original branches)

$$2) \quad \begin{array}{c} S_c \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array} \quad \equiv \quad \begin{array}{c} S_a + S_b \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array} \quad \text{sum of original branches}$$

$$3) \quad \begin{array}{c} S_c \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array} \quad \equiv \quad \begin{array}{c} S_a \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array} \quad | \quad \text{"self loop"}$$

$$\left. \begin{aligned} C &= S_a a_1 + S_b C \rightarrow a_1 = \frac{S_a}{1 - S_c} C \\ b_1 &= S_b C \end{aligned} \right\} \quad \left. \begin{aligned} b_1 &= \frac{S_a S_b}{1 - S_c} C \end{aligned} \right\}$$

4) "splitting rule"

$$\begin{array}{c} S_c \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array} \quad \equiv \quad \begin{array}{c} S_a \\ \text{---} \\ a_1 \end{array} \quad \begin{array}{c} S_c \\ \text{---} \\ b_1 \end{array} \quad | \quad \begin{array}{c} S_b \\ \text{---} \\ b_1 \end{array}$$

Mason's rule: Solving linear equation by inspecting SFG and involving Mason's rule.

o Definitions:

- 1) path: series of branches, in the direction of arrows along which no node is crossed more than once.
- 2) loop:
 - 2.1) 1st-order-loop: product of branches encountered in a journey starting from a node moving along which
 - 2.2) 2nd-order-loop: product of ≥ 2 non-touching loops
 - 2.3) nth-order-loop: product of ≤ n non-touching loops.
- 2.4) non-touching loop(s) in the system that not touch each other(s).

Mason's Rule:

ratio of interest

$$T = \sum_k G_k \frac{\Delta k}{\Delta}$$

gain of path k


Δ_k : cofactor of path k: $\Delta_k = 1 - \Sigma L^k(1) + \Sigma L^k(2) - \dots$

$\Sigma L^k(n)$: sum of all nth open loops

not touching path k.

$= 1 - \Sigma L(1) + \Sigma L(2) - \Sigma L(3) + \dots$

Example 1 Find b_i/a_j :

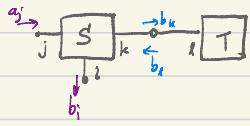


$$\sum_k G_k \frac{\Delta k}{\Delta} = \frac{b_i}{a_j} = \frac{S_{ij}}{1-S_{ii}T_{ii}} + \frac{S_{ij}T_{ii}S_{ik}}{1-S_{kk}T_{kk}} \Rightarrow S_{ij} + \frac{S_{ij}T_{ii}S_{ik}}{1-S_{kk}T_{kk}}$$

non-touching loops: $\Delta = 1 - S_{ii}T_{ii}$


non-touching loops: $A = 1 - S_{ii}T_{ii}$

$\Delta_2 = 1$

Example 2

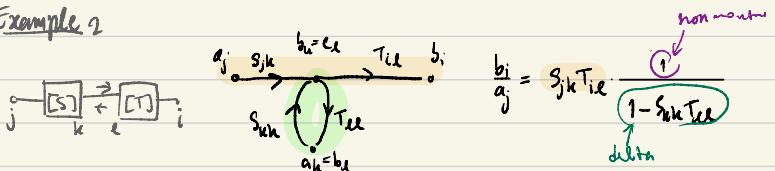


Examples:

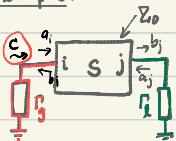

b_i/c (not b_i/a_j)

$$a_i = c + b_i P_g$$

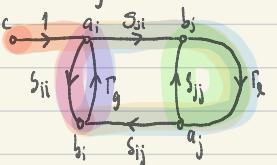

1) Path: $S_{ii}, S_{ji} P_g S_{ij}$

2) Loops:

- 1st order loops: $S_{ii} P_g, S_{jj} P_g, S_{ij} P_g S_{ji}$

- a product of any 2 non-touching 1st order loops

$$P_g = S_{ii} P_g S_{jj} P_g$$

$$\Delta = 1 - (S_{ii} P_g + S_{jj} P_g + S_{ii} P_g S_{ji} P_g) + S_{ii} P_g S_{jj} P_g$$

$$\Delta = (1 - P_g S_{ii})(1 - P_g S_{jj}) - S_{ji} P_g S_{ij} P_g$$

$$G_1: S_{ii} \Rightarrow \Delta_1 = 1 - S_{ii} P_g$$

$$G_2: S_{ji} P_g S_{ij} \Rightarrow \Delta_2 = 1$$

$$\frac{b_i}{c} = \frac{G_1 \Delta_1 + G_2 \Delta_2}{\Delta}$$

Wave source

source in lower-freq circuits

o Thvenin equivalent




Z_g : Thvenin input impedance.

V_{oc} : open circuit gain

r_g : generator reflection coefficient

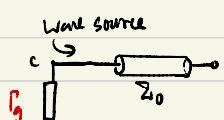C: incident wave amplitude generator.
(when connect to a matched load).




P_g : need to specify Z_{in} (normalized impedance)

$$P_g = \frac{Z_g - Z_0}{Z_g + Z_0}, \quad C = \frac{V_{oc}}{\sqrt{Z_0 + Z_g}} = \frac{V_{oc}}{\sqrt{Z_0}} \frac{\sqrt{Z_0 + Z_g}}{\sqrt{Z_0 + Z_g}} = \frac{V_{oc}}{Z_0 + Z_g}$$

function Z_{in}

Example

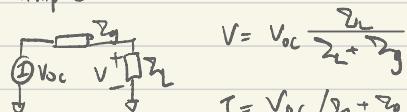

$$V = V_{oc} \frac{Z_L}{Z_L + Z_g}$$

$$I = V_{oc} / (Z_L + Z_g)$$

$$P_L = \text{Re} \{ V Z^* \} = |V_{oc}|^2 \frac{Z_L}{|Z_L + Z_g|^2}$$



Power delivered to load

$$P_L = |A|^2 |B|^2 = |A|^2 (1 - |P_g|^2)$$

$$P_L = \frac{|C|^2 (1 - |P_g|^2)}{|1 - P_g P_g^*|^2}, \quad C = \frac{V_{oc} \sqrt{Z_0}}{Z_0 + Z_g}, \quad P_g = \frac{Z_g - Z_0}{Z_g + Z_0}, \quad P_g = \frac{Z_g - Z_0}{Z_g + Z_0}$$

$$1 - |P_g|^2 = 1 - P_g P_g^*$$

$$= \frac{2Z_0 (Z_L + Z_g)}{(Z_L + Z_0)^2}$$

$$1 - P_g P_g^* = \frac{2Z_0 (Z_g + Z_0)}{(Z_g + Z_0)^2}$$

$$P_L = \frac{|V_{oc}|^2 Z_0}{(Z_0 + Z_g)^2} \cdot \frac{2Z_0 (Z_g + Z_0)}{(Z_g + Z_0)^2} \cdot \frac{1}{|Z_L + Z_g|^2} \cdot \frac{1}{4Z_0 (Z_g + Z_0)^2} \Rightarrow P_L = \frac{|V_{oc}|^2 (Z_L + Z_g)}{4Z_0 (Z_g + Z_0)^2}$$

$$P_L = \frac{|V_{oc}|^2 (Z_L + Z_g)}{4Z_0 (Z_g + Z_0)^2}$$