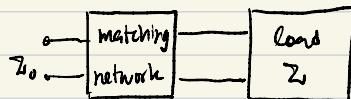


Impedance Matching (Pozar ch.5)




Example:

- Max power delivery

- Better SNR

- Antenna array, reduce amplitude and phase error in distributed networks

• Matching network examples

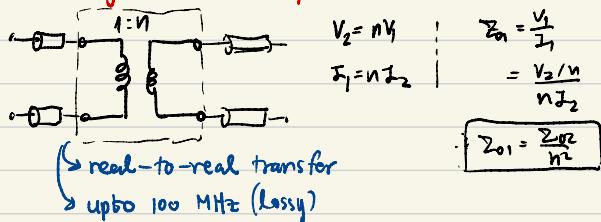

Usually matching network uses lossless elements (L/C or transmission line)

↑ avoid energy dissipation \Rightarrow tend to have

narrower bandwidth.

lossy elements, e.g.




L.C. element matching (Pozar 5.1)

- Advantage: less space, better bandwidth (compared to TL)

- Disadvantage: primarily used < 30 GHz

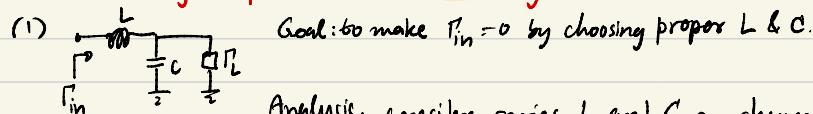
Consider two cases: using lumped L-section matching network



Analysis: consider series L and C can change reactance of Z_L for a matched network.


Strategy: use shunt C to move r_L along constant conductance circle to lower half of $r=1$ circle.
then choose L to tune out residue reactance.

Forbidden regions

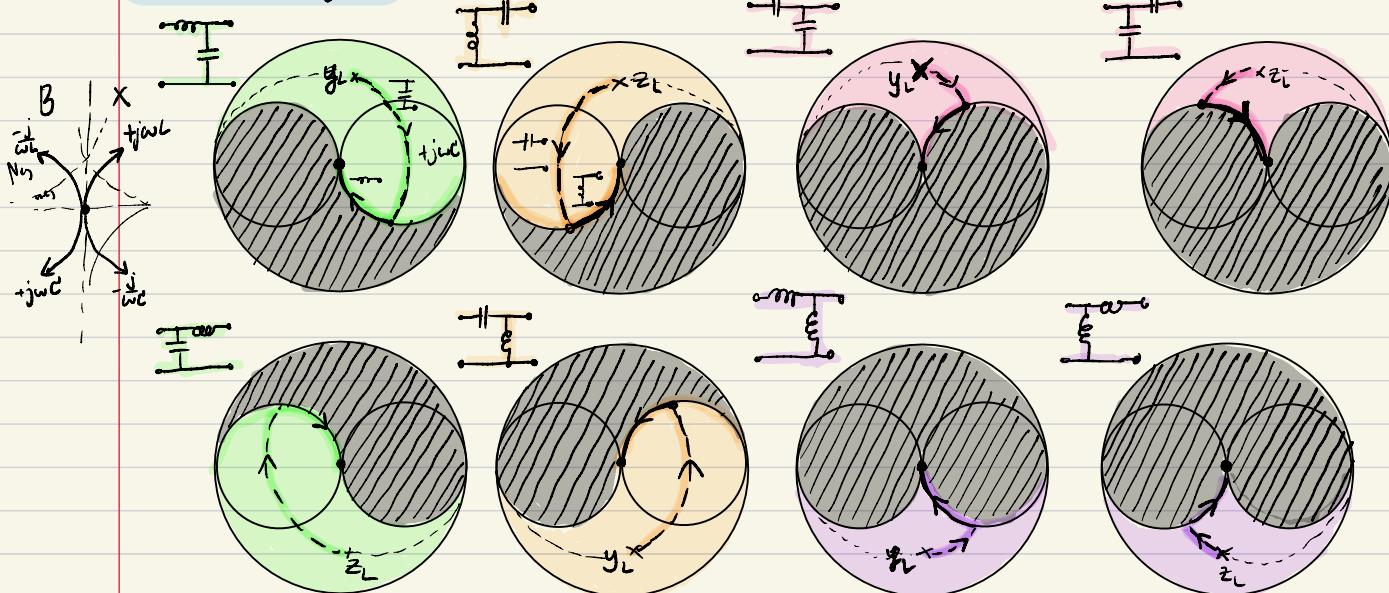

LC matching \Rightarrow lossless, easy, compact but sacrifices BW

Series L parallel circuit

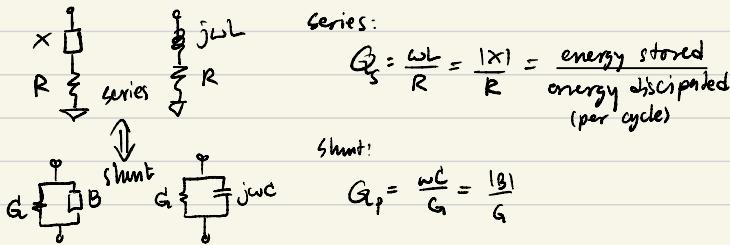

\rightarrow know X and R , find equivalent G_p and B_p

$$Z = R + jX_s = \frac{1}{Y_p} = \frac{1}{G_p + jB_p} \quad \& \quad T_p = G_p + jB_p = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$



$$\hookrightarrow G_p = \frac{R}{R^2 + X^2} = \frac{1}{R} \frac{1}{1 + Q_s^2} \quad \& \quad B_p = -\frac{X}{R^2 + X^2} = -\frac{1}{X} \frac{1}{1 + Q_s^2}$$

\rightarrow know G and B , find equivalent R_s and X_s

$$Y = G + jB = \frac{1}{Z_s} = \frac{1}{R_s + jX_s} \Rightarrow R_s + jX_s = \frac{1}{G + jB} = \frac{G - jB}{G^2 + B^2}$$

$$\therefore R_s = \frac{G}{G^2 + B^2} = \frac{1}{G} \frac{1}{1 + (\frac{B}{G})^2} = \frac{1}{G} \frac{1}{1 + Q_p^2} \quad \& \quad X_s = -\frac{B}{G^2 + B^2} = -\frac{1}{B} \left(\frac{1}{1 + Q_p^2} \right)$$

Impedance transformation

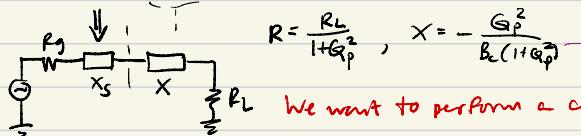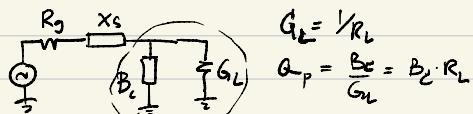

We want to perform a conjugate matching:

$$R = R_g \text{ and } X = -X_s$$


$$\Rightarrow 1 + G_p^2 = \frac{R_L}{R_g} \Rightarrow G_p = \sqrt{\frac{R_L}{R_g} - 1}$$

$$\text{solution: } B_c = \frac{G_p}{R_L} = \frac{1}{R_L} \sqrt{\frac{R_L}{R_g} - 1}$$

$$X_s = R_g \sqrt{\frac{R_L}{R_g} - 1}$$

Note: under the matching condition: $G_{L'} = G_p$
 $G_p = B_c R_L = \frac{B_c}{G_L} = \sqrt{\frac{R_L}{R_g} - 1} = Q_s = \frac{X_s}{R}$

Feb 26, 2025

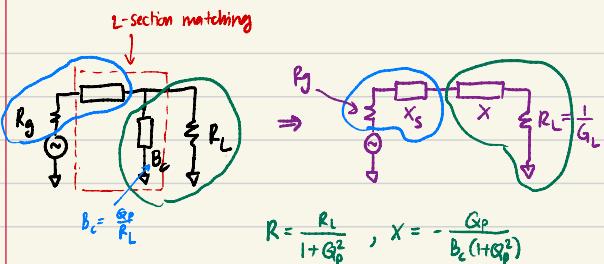

$$R_g = \frac{R_L}{1 + Q_p^2} \Rightarrow 1 + Q_p^2 = \frac{R_L}{R_g} \Rightarrow Q_p = \sqrt{\frac{R_L}{R_g} - 1}$$

$$\begin{aligned} B_L &= \frac{Q_p}{R_L} = \frac{1}{R_L} \sqrt{\frac{R_L}{R_g} - 1} \\ X_S &= R_S \sqrt{R_L/R_g - 1} \end{aligned} \quad \left\{ R_L = R_g \right.$$

$$Q_S = Q_p : Q_p = B_L R_L = \sqrt{\frac{R_L}{R_g} - 1} = \frac{X_S}{R_g} = Q_S$$

Remark: the parallel-series transformation



$$Q_S = \frac{|X|}{R}$$

$$Q_p = \frac{1}{R} \left(\frac{1}{1 + Q_S^2} \right)$$




$$Q_p = \frac{|B|}{G}$$

$$R_S = \frac{1}{G} \left(\frac{1}{1 + Q_p^2} \right)$$

$$X_S = -\frac{1}{B} \left(\frac{Q_p^2}{1 + Q_p^2} \right)$$

G and bandwidth

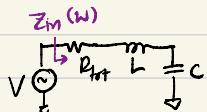"effective" G of circuit is given by $G_e = \omega \frac{U}{P_L}$ overall energy storage
series resonant circuit as example:



$$\begin{aligned} Z_{in}(\omega) &= R_{tot} + j\omega L - j\frac{1}{\omega C} \\ &= R_{tot} + j\omega L \left(1 - \frac{1}{\omega^2 LC} \right) \\ &= R_{tot} + j\omega L \left(\frac{\omega^2 - \omega_0^2}{\omega^2} \right) \quad \omega_0 = \frac{1}{\sqrt{LC}} \text{ resonant freq. of circuit.} \end{aligned}$$

zoom in section

$$\begin{aligned} \omega^2 - \omega_0^2 &= (\omega - \omega_0)(\omega + \omega_0) \\ &= \Delta\omega(2\omega + \Delta\omega) \approx 2\omega(\Delta\omega) \end{aligned}$$

$$\begin{aligned} Z_{in}(\omega) &= R_{tot} + j\omega L \left(\frac{2\omega \Delta\omega}{\omega^2} \right) \\ &= R_{tot} + j \cdot 2\Delta\omega L \end{aligned}$$

At resonance: $P_0 = \frac{|V|^2}{R_{tot}}$ At "half-power" point (3dB)

(RMS notation)


$$P_{\frac{1}{2}} = \frac{1}{2} P_0 = \frac{1}{2} \frac{|V|^2}{R_{tot}} = \frac{|V|^2}{|Z_{in, \frac{1}{2}}|^2 \cdot R_{tot}}$$

$$|Z_{in, \frac{1}{2}}(\omega)|^2 = 2R_{tot}^2$$

$$R_{tot}^2 + (2\Delta\omega L)^2 = 2R_{tot}^2$$

$$1\Delta\omega L = \frac{1}{2} \frac{R_{tot}}{L} = \frac{1}{2} \cdot \frac{\omega_0}{Q}$$
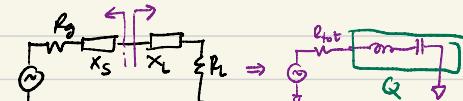
$$\text{Thus, } \frac{2\Delta\omega L}{\omega_0} = \frac{4\Delta f_{FWHM}}{f_0} = \frac{1}{Q}$$



$$FBW = \frac{2\Delta\omega}{\omega} = \frac{4\Delta f_{FWHM}}{f_0} = \frac{1}{Q}$$

$$Q = \frac{\omega_0 L}{R_{tot}} = \frac{\omega_0 L}{R_{tot}/2} \cdot \frac{1}{2} = \frac{Q_0}{2} = \frac{1}{2} \sqrt{\frac{R_L}{R_g} - 1}$$


$$\Rightarrow FBW = \frac{2}{\sqrt{\frac{R_L}{R_g} - 1}}$$

What if we want narrower FBW?





match up and turn down to get high current ratio.

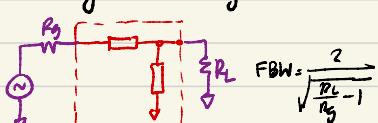Comment: Given that we have only two independent parameters (R_L, R_g) to control Q (FBW) to design matching network with different Q, need to add more components.




- Narrow band : e.g. $10\Omega \rightarrow 100\Omega \rightarrow 50\Omega$
- Wide band : e.g. $10\Omega \rightarrow 20\Omega \rightarrow 30\Omega \rightarrow 50\Omega$

Design with different Q:

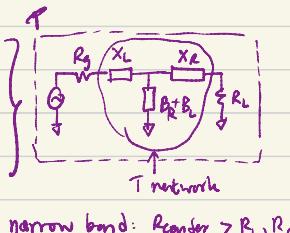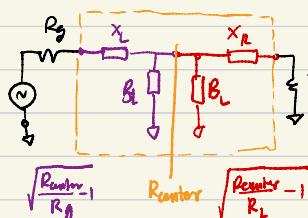


narrow band: $R_{center} > R_L, R_g$

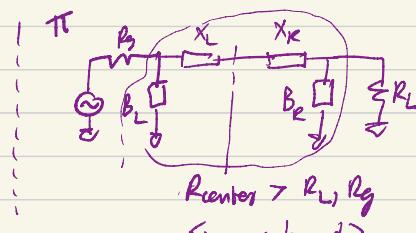

narrow band

Broader band matching

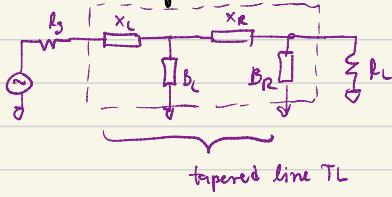

Cascaded L-section

can broaden BW
w/ matching networks

Design matching network with a given Q

→ Strategy: plot a contour Q circle on the Smith Chart.


$$\text{Recall } G_m = \frac{|X|}{R} \quad \text{normalized} \quad \Rightarrow \quad Z = \frac{1 + j\Gamma}{1 - j\Gamma} = \frac{(1 - Q^2)^{1/2} + jQ}{(1 + Q^2)^{1/2} - jQ} = r + jx \quad \text{if } \frac{X}{R} = \frac{2V}{1 - Q^2} = \pm Q_m$$

$$r^2 + x^2 - 1 \pm \frac{2V}{Q_m} = 0$$

$$V^2 + (VQ_m)^2 = \frac{1 + Q_m^2}{Q_m^2}$$


$$\text{Center: } (0, \pm \frac{1}{Q_m})$$

$$\text{radius} = \frac{\sqrt{1+Q_m^2}}{Q_m}$$

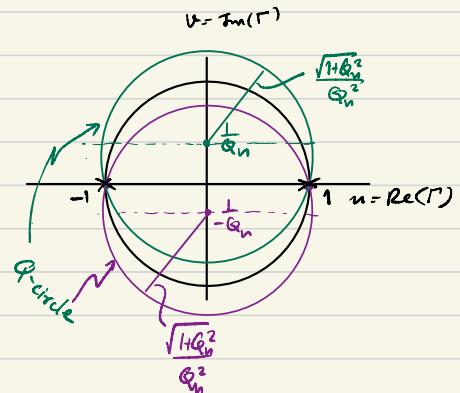


Mar 3

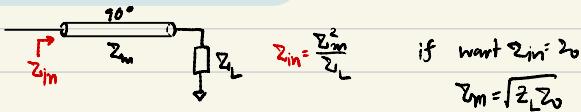Quarter-wave transformer Polar S-parameters




$$\text{if want } Z_m = 2Z_L \quad Z_m = \sqrt{2}Z_L$$

① If Z_m is not practical.

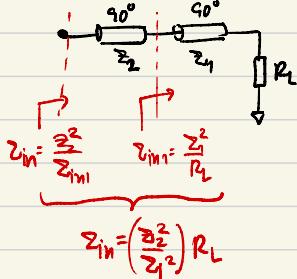


relative: can be any values that provide an appropriate ratio.

② Complex load

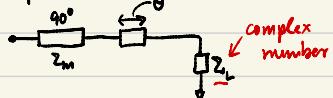

Use the first transmission line to translate Z_L to a real (resistive) impedance

Partial reflection

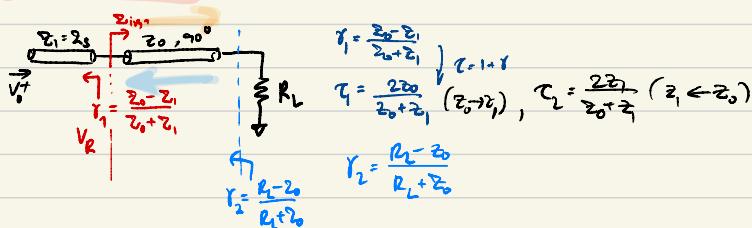

$$V_R = V_0^+ r_1 + V_0^+ r_1 (-j) r_2 (-j) \tau_2 \\ + V_0^+ \tau_1 (-j) r_2 (-j) (-r_1) (-j) r_1 (-j) \tau_1$$

$$\begin{aligned} \Gamma_{\text{total}} &= \frac{V_R}{V_0^+} = r_1 - \tau_1 \tau_2 r_2 - \tau_1 \tau_2 r_1 r_2^2 - \tau_1 \tau_2 r_1^2 r_2^3 - \dots \\ &= r_1 - \tau_1 \tau_2 r_2 (1 + r_1 r_2 + r_1^2 r_2^2 + \dots) \\ &= r_1 - \tau_1 \tau_2 r_2 \sum_{n=0}^{\infty} (r_1 r_2)^n \\ &= r_1 - \frac{\tau_1 \tau_2 r_2}{1 - \tau_1 \tau_2} \\ \Gamma_{\text{tot}} (1 - \tau_1 \tau_2) &= r_1 - r_1^2 r_2 - \tau_1 \tau_2 r_2 \\ &= r_1 - r_2 (r_1^2 + \tau_1 \tau_2) \end{aligned}$$

$$\gamma_1 = \frac{z_0 - z_1}{z_0 + z_1}, \quad \gamma_2 = \frac{z_0 - z_2}{z_0 + z_2}, \quad \gamma_L = \frac{z_0 - z_L}{z_0 + z_L}$$

$$\therefore \gamma_1^2 + \gamma_2 \gamma_L = \frac{(z_0 - z_1)^2 + (z_0 - z_2)(z_0 - z_L)}{(z_0 + z_1)^2} = 1$$

$$\left. \begin{aligned} \Gamma_{\text{tot}}(1 - \gamma_1 \gamma_2) &= \gamma_1 - \gamma_2 \\ &= \frac{z_0 - z_1}{z_0 + z_1} - \frac{z_0 - z_L}{z_0 + z_L} \\ &= \frac{s(z^2 - z_1 z_L)}{(z_0 + z_1)(z_0 + z_L)} \end{aligned} \right\}$$

$$\text{We want } \Gamma_{\text{tot}} = 0 \Rightarrow z_0^2 = z_s R_L \Rightarrow z_0 = \sqrt{z_s R_L}$$

BW of quarter-wave transformer:




$$\Gamma_{in} = \frac{z_{in} - z_0}{z_{in} + z_0} \Rightarrow \Gamma_{in}(\theta) = \frac{z_m(R_L - z_0) + j(z_m^2 - z_0 z_L) \tan \theta}{z_m(R_L + z_0) + j(z_m^2 + z_0 z_L) \tan \theta}$$

$$\Gamma_{in}(\theta) = \frac{R_L - z_0}{(R_L + z_0) + j \sqrt{R_L z_0} \tan \theta}$$

$$|\Gamma_{in}(\theta)| = \frac{|R_L - z_0|}{\sqrt{(R_L + z_0)^2 + 4 z_0 R_L \tan^2 \theta}} \quad \text{for } \theta = \frac{\pi}{2} \text{ (quarter-wave transformer)}$$

$$\hookrightarrow \theta = \frac{\pi}{2} : |\Gamma_{in}(\theta)| \sim \frac{|R_L - z_0|}{2 \sqrt{z_0 R_L}} | \cot \theta |$$

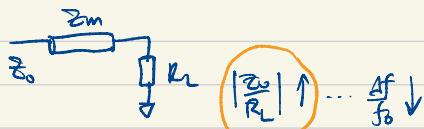


Disparity between R_L and Z_m decides BW

↪ larger disparity \rightarrow narrower BW

$\theta = \frac{\pi}{2}$ cut design freq.

↪ varying freq. \rightarrow pl differs from $\frac{\pi}{2} \Rightarrow$ mismatch.

Bandwidth matching (Power S.S.)

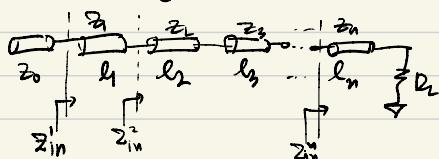

Define Z_{in}^N = impedance looking into Nth section

$$Z_{in}^N = Z_N \frac{R_L + j z_N \tan \theta}{z_N + j R_L \tan \theta} \quad \tan \theta = \frac{\sin \theta}{\cos \theta} = -j \frac{e^{j\theta} - e^{-j\theta}}{e^{j\theta} + e^{-j\theta}}$$

$$= Z_N \frac{(R_L + z_N) e^{j\theta} + (R_L - z_N) e^{-j\theta}}{(R_L + z_N) e^{j\theta} - (R_L - z_N) e^{-j\theta}}$$

$$= Z_N \frac{e^{j\theta} + \gamma_N e^{-j\theta}}{e^{j\theta} - \gamma_N e^{-j\theta}}$$

Define mismatch factor

$$\gamma_N = \frac{R_L - z_N}{R_L + z_N}$$

(sectional reflection coefficient)

$$\Gamma_{N+1} = \frac{Z_{in}^N - Z_{in} + Z_{in}(e^{j\theta} + \gamma_N e^{-j\theta}) - Z_{in}(e^{j\theta} - \gamma_N e^{-j\theta})}{Z_{in}^N + Z_{in-1} - Z_{in}(e^{j\theta} + \gamma_N e^{-j\theta}) + Z_{in-1}(e^{j\theta} - \gamma_N e^{-j\theta})}$$

$$= \frac{(Z_N - Z_{N+1}) e^{j\theta} + \gamma_N (Z_N + Z_{N+1}) e^{-j\theta}}{(Z_N + Z_{N+1}) e^{j\theta} + \gamma_N (Z_N - Z_{N+1}) e^{-j\theta}}$$

$$= \frac{\gamma_{N+1} + \gamma_N e^{-j2\theta}}{1 + \gamma_N \gamma_{N+1} e^{j2\theta}}$$

$$\Gamma_{N+1} = \frac{Z_N - Z_{N+1}}{Z_N + Z_{N+1}}$$

$$\Gamma_N = \gamma_N$$

$$\Gamma_{N+1} = \gamma_{N+1} + \gamma_N e^{-j2\theta}$$

$$\Gamma_{N+2} = \gamma_{N+2} + \gamma_{N+1} e^{-j2\theta} = \gamma_{N+2} + \gamma_{N+1} e^{j2\theta} + \gamma_N e^{-j4\theta}$$

Theory of small reflection: assume mismatch factor $\ll 1 \Rightarrow \Gamma_{N+1} = \gamma_{N+1} + \gamma_N e^{-j2\theta}$

$$\Gamma = \gamma_1 e^{j\theta} + \dots + \gamma_N e^{j2\theta}$$

↪ mismatch between adjacent transmission lines is small.

$$\Gamma = \sum_{n=0}^N \gamma_n e^{-jn\theta}, \quad \gamma_n = \frac{z_{n+1} - z_0}{z_{n+1} + z_0}$$

\Rightarrow choose γ_n such that $|\Gamma|$ minimize over a wide frequency range (BW matching)


let $w = e^{j\omega}$

$$\Rightarrow \Gamma = \gamma_0 + \gamma_1 w + \gamma_2 w^2 + \dots + \gamma_N w^N$$

$$\boxed{\Gamma = \gamma_N \prod_{n=1}^N (w - w_n)}, \quad w_n \Rightarrow n^{\text{th}} \text{ zero of polynomial.}$$

$\hookrightarrow N$ degrees of freedom

Diagram of a ladder network with R_L and Z_0 . If $\theta = 0 \Rightarrow \Gamma = \frac{R_L - Z_0}{R_L + Z_0} = \sum_{n=0}^N \gamma_n$ ($w=1$)

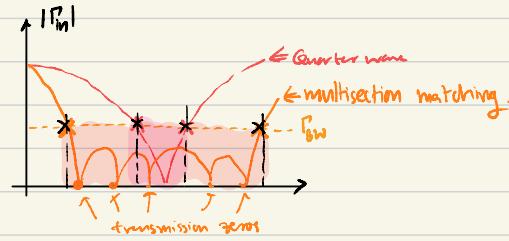

Cases:

- ① Uniform mismatch factor: $\gamma_N = \gamma_n$
- ② Maximally flat - Binomial transformer (Butterworth)
- ③ Chebychev (Max BW)



① Uniform mismatch factor: $\gamma_N = \gamma_n$

$$\Gamma = \gamma_N (1 + w + w^2 + \dots + w^N)$$

$$\frac{\Gamma}{\gamma_N} = \frac{w^{N+1} - 1}{w - 1} = \frac{w^{\frac{N+1}{2}} (w^{\frac{N+1}{2}} - w^{-\frac{N+1}{2}})}{w^{\frac{1}{2}} (w^{\frac{1}{2}} - w^{-\frac{1}{2}})}, \quad w = e^{-j2\theta}$$


$$= w^{\frac{N}{2}} \frac{\sin[(N+1)\theta]}{\sin\theta} = e^{-j\theta} \frac{\sin((N+1)\theta)}{\sin\theta}$$

Boundary condition: $\theta = 0 \Rightarrow \Gamma(\theta=0) = \frac{R_L - Z_0}{R_L + Z_0} = \sum_{n=0}^N \gamma_n = (N+1)\gamma_N$

$$\gamma_N = \frac{1}{N+1} \frac{R_L - Z_0}{R_L + Z_0}$$

$$\Gamma = \gamma_N e^{-jN\theta} \frac{\sin[(N+1)\theta]}{\sin\theta} = \frac{1}{N+1} \frac{R_L - Z_0}{R_L + Z_0} e^{-jN\theta} \frac{\sin[(N+1)\theta]}{\sin\theta}$$

$$|\Gamma| = \left| \frac{R_L - Z_0}{R_L + Z_0} \right| \left| \frac{\sin[(N+1)\theta]}{(N+1)\sin\theta} \right|$$

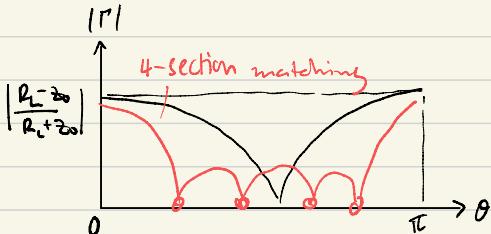


Remark

- ① $|\Gamma|$ pattern repeats every π
- ② For N -sections hence N -min and $N-1$ ripples
- ③ zero at $\theta = \frac{n\pi}{N+1}$

② Binomial transformer \rightarrow maximally flat \rightarrow choose all zeros at the center.
(to be cont.)

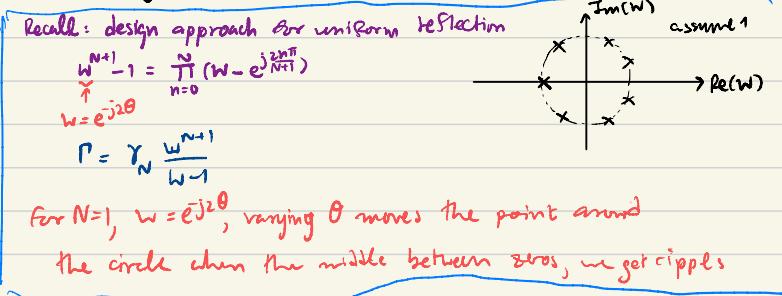Max flat matching network \rightarrow Butterworth / Binomial



\Rightarrow How to reduce the ripples?

\hookrightarrow One effective way is to design multiple zeros at the same point
 \Rightarrow changing Σ of each section

\Rightarrow Binomial transformer \Rightarrow chose all zeros $w_n = -1$

$$\Gamma = \gamma_N (w + 1)^N \text{ Expand with binomial theorem}$$

$$\Gamma = \gamma_N (w^n + Nc_1 w^{n-1} + \dots + \frac{N!}{(N-n)!n!} w^{n-n} + \dots + 1)$$

γ_N combination
 $C_n^N = \binom{N}{n} = \frac{N!}{(N-n)!n!}$

$$\Gamma(\theta) = \gamma_N (e^{j2\theta} + 1)^N = \gamma_N (e^{j\theta} (e^{j\theta} + e^{-j\theta}))^N$$

$$= \gamma_N e^{j2\theta} (2\cos\theta)^N \quad (\Gamma(0) = Z^N \gamma_N \frac{R_L - Z_0}{R_L + Z_0})$$

$$|\Gamma(\theta)| = \frac{R_L - Z_0}{R_L + Z_0} |\cos\theta|^N$$

loss ripples:
at the cost of achievable BW



\Rightarrow Chebyshev transformer (Power S7) more BW at the cost of more ripples


Design example = 5GHz Binomial transformer with 4 sections match from $100 \Omega \rightarrow 50 \Omega$

1) Evaluate:

$$2^N \gamma_N = \frac{R_L - Z_0}{R_L + Z_0} = \frac{100 - 50}{100 + 50} = \frac{1}{3}$$

$$N=4 \rightarrow 2^4 \gamma_4 = \frac{1}{3} \Rightarrow \gamma_4 = \frac{1}{3} \cdot \frac{1}{16} = \frac{1}{48}$$

2) For binomial transformer

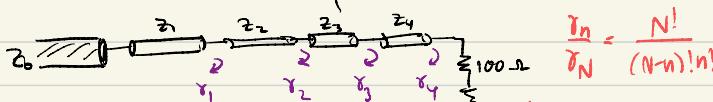

$$\frac{\gamma_n}{\gamma_N} = \frac{N!}{(N-n)!n!}$$

$$\text{① } \gamma_4 = \gamma_4 \frac{4!}{(4-4)!4!} = \frac{1}{48} = \frac{R_L - Z_4}{R_L + Z_4} \Rightarrow Z_4 = 95.9 \Omega$$

$$\text{② } \gamma_3 = \gamma_4 \frac{3!}{(4-3)!3!} = \frac{1 \cdot 4}{48} = \frac{1}{12} = \frac{Z_4 - Z_3}{Z_4 + Z_3} \Rightarrow Z_3 = 81.2 \Omega$$

$$\text{③ } \gamma_2 = \gamma_4 \frac{2!}{(4-2)!2!} = \frac{1}{48} \cdot 6 = \frac{1}{8} = \frac{Z_3 - Z_2}{Z_3 + Z_2} \Rightarrow Z_2 = 63.2 \Omega$$

$$\text{④ } \gamma_1 = \frac{1}{48} \cdot 4 = \frac{1}{12} = \frac{Z_2 - Z_1}{Z_2 + Z_1} \Rightarrow Z_1 =$$

Self-consistent matching

$$\Gamma = \sum_{n=0}^N \gamma_n e^{-jn\theta}, \quad \gamma_n = \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$


Power series approx

$$\ln \frac{Z_{n+1}}{Z_n} \approx 2 \frac{Z_{n+1} - Z_n}{Z_{n+1} + Z_n}$$

$$\therefore \gamma_n = \frac{1}{2} \ln \frac{Z_{n+1}}{Z_n}$$

Stub matching

Recall

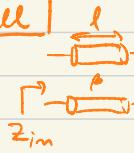


$$Z_{in} = jY_s \tan \theta$$



$$Z_{in} = -j \cot \beta l$$

Series stub tuning

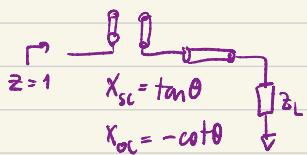


①


② Maximize

To maximize BW , for given termination, choose a shorter one

③ Multiple solutions

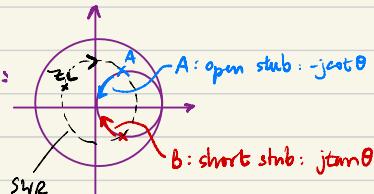

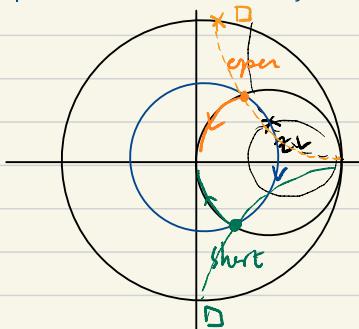Example: match $Z = 2 + j1.6$, series open stub.




① Find z_L value on the chart


② Drawing SWR circle for z_L

③ Find intercept values $z=1$


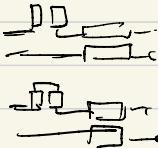
④ Two cases $\begin{cases} 1+j\Delta \rightarrow \text{open stub (series)} \\ 1-j\Delta \rightarrow \text{short stub (series)} \end{cases}$




Short stub is easier for higher freq

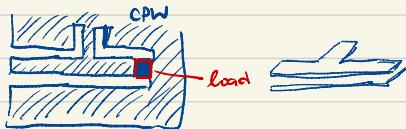

Shunt stub

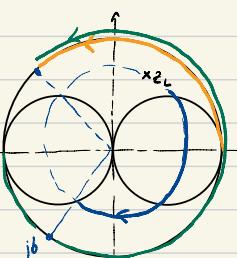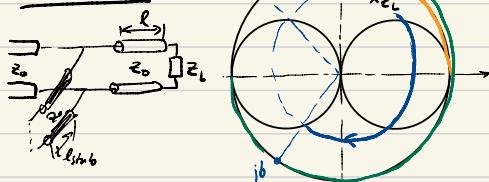

Double stub (Pozar 5.3)

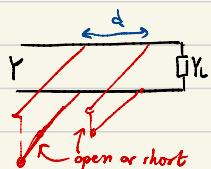


Advantage: tunable stub in coax

Disadvantage: not matching all impedance

Example in Pozar book


Tapered Line (Pozar 5.8)

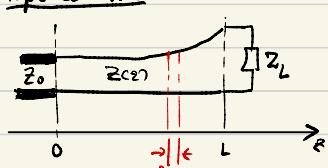


$$\frac{dI}{dz} = \frac{2 + j2\pi - j}{Z_0 + j2\pi - j} \quad \left. \begin{array}{l} \text{small reflection} \\ |dI|^2 = \frac{dI}{dz} \cdot \frac{dI}{dz}^* = \frac{1}{2} \frac{d(\ln(Z_0/Z_L))}{dz} \end{array} \right\}$$

\Rightarrow Example: exponential taper
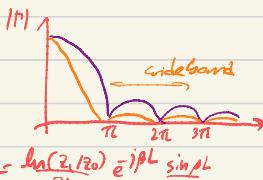
$$\begin{aligned} Z_{c(t)} &= Z_0 e^{-rt^2/2L} \\ r &= \frac{1}{L} \ln\left(\frac{Z_L}{Z_0}\right) \end{aligned} \quad \left. \begin{array}{l} r = \frac{1}{2} \int_0^L e^{-rt^2/2L} \frac{d(\ln(Z_0/Z_L))}{dt} dt = \frac{\ln(Z_0/Z_L)}{2L} e^{j\beta L} \end{array} \right\}$$



Bode-Fano Criterion (Pozar 5.9)

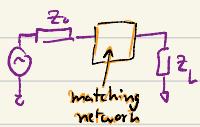

What is the theoretical limit
of the matching network?

Review

- Smith chart: plot of Γ on the complex plane.

- Lumped element based impedance matching

→ LC ladder impedance matching (forbidden region)

→ $Q = \sqrt{\frac{R_s}{R_L} - 1}$, BW limitation

→ π and T network for control of Q

- T-line based matching

→ Quarter-wave transformer: $Z_{in} = \frac{Z_0^2}{Z_L}$

→ Broadband matching

 └ Theory of small reflection

 └ Multi-section transformer

 - Uniformly distributed section

 - Binomial transformer (flat band) \Rightarrow Butterworth

 - Chebyshev transformer (skip)

 └ Real Load

→ Stub tuning

 - Single stub tuning: series/shunt
 open/shunt

 └ Complex load

 - Choice of stub: favor shortest T-line

 - Double stub tuning (skip)

→ Other topics

 - tapered line \hookrightarrow super wideband real load

 - Theoretical limit