
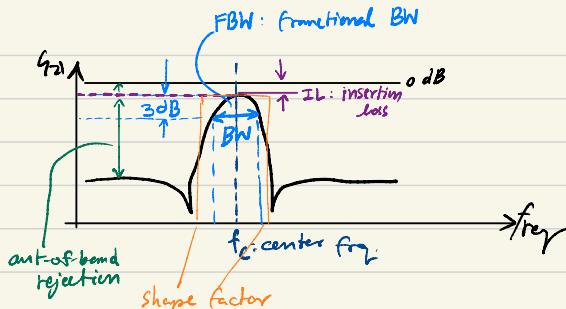


Microwave Filter (Pozar chapter 8)

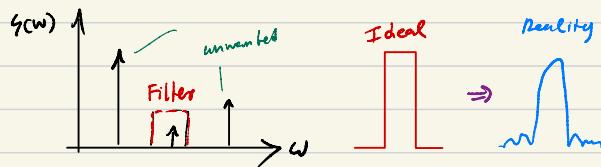

Topics

① Properties of $\Gamma(\omega)$ and $Z(\omega)$ in freq. domain (Pozar 4.1)

② Insertion loss method (Pozar 8.2)

 └ LPF transform
 └ BPF
 └ SF

③ Filter transformation (Pozar 8.4) : LPF $\xrightarrow{\text{BPF}}$ BPF
 └ SF

④ Filter implementation

Properties (freq response) of $\Gamma(\omega)$, $Z(\omega)$

$$v(t) \xrightarrow{\mathcal{F}} V(\omega) \quad \left\{ \begin{array}{l} v(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} V(\omega) e^{j\omega t} d\omega \\ \text{real: } v(t) = v^*(t) \end{array} \right.$$

$$v^*(t) = \frac{1}{2\pi} \int_{-\infty}^{\infty} V^*(\omega) e^{-j\omega t} d\omega \quad \begin{array}{l} \text{replace } \omega \\ \text{by } -t \end{array} = \frac{1}{2\pi} \int_{-\infty}^{\infty} V(-\omega) e^{j\omega t} d\omega$$

$$\begin{aligned} V(\omega) &= \operatorname{Re}(V(\omega)) + j\operatorname{Im}(V(\omega)) \quad \left\{ \begin{array}{l} \operatorname{Re}(V(\omega)) \text{ is even function} \\ \operatorname{Im}(V(\omega)) \text{ is odd function} \end{array} \right. \\ V(-\omega) &= \operatorname{Re}(V(\omega)) - j\operatorname{Im}(V(\omega)) \end{aligned}$$

Similarly:
 $\operatorname{Re}(\Gamma(\omega))$ is even function.
 $\operatorname{Im}(\Gamma(\omega))$ is odd function.

$$V(\omega) = Z(\omega) I(\omega)$$

$$\begin{aligned} &= [R(\omega) + jX(\omega)] \cdot [I_p(\omega) + jI_i(\omega)] \\ &= [R(\omega) I_p(\omega) - X(\omega) I_i(\omega)] + j[X(\omega) I_p(\omega) + R(\omega) I_i(\omega)] \\ &\quad \begin{array}{c} \text{even} \quad \text{even} \\ \text{odd} \quad \text{odd} \end{array} \end{aligned}$$

Thus:
 $R(\omega)$ is even
 $X(\omega)$ is odd

$$\Gamma(\omega) = \frac{Z(\omega) - Z_0}{Z(\omega) + Z_0} = \frac{R(\omega) - Z_0 + jX(\omega)}{R(\omega) + Z_0 + jX(\omega)}$$

$$\Gamma(-\omega) = \frac{R(-\omega) - Z_0 + jX(-\omega)}{R(-\omega) + Z_0 + jX(-\omega)} = \frac{R(\omega) - Z_0 - jX(\omega)}{R(\omega) + Z_0 - jX(\omega)}$$


$$\Gamma(-\omega) = \Gamma^*(\omega)$$

$$|\Gamma(\omega)| = \Gamma(\omega) \cdot \Gamma^*(\omega) = \Gamma(\omega) \cdot \Gamma(-\omega) = |\Gamma(-\omega)|^2 \Rightarrow |\Gamma(\omega)|^2 \text{ is even function}$$

$\Rightarrow \Gamma(\omega)$ is even function,

we can do this
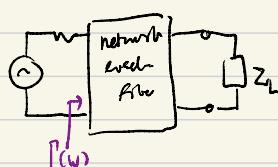
$$\Gamma(\omega) = a + b\omega + c\omega^2 + d\omega^3 + \dots = \sum_{n=0}^{\infty} a_n \omega^n$$



Insertion Loss:

$$IL = \frac{P_{av}}{P_L} \leftarrow \begin{array}{l} \text{power available} \\ \text{power delivered to load} \end{array}$$

$$IL = \frac{1}{1 - |\Gamma(\omega)|^2}$$

$$IL = 1 + \frac{M(\omega)}{N(\omega)} \Rightarrow \text{replace by LC network}$$

May 31

$$|\Gamma(\omega)|^2 \rightarrow \text{even function}$$

↓
Insertion loss method:

 $I_L = \frac{1}{1 - |\Gamma(\omega)|^2}$

Available power:

$$P_{av} = \frac{|V|^2}{4Z_0}$$

Delivered power:

$$P_L = \frac{V}{Z_0 + Z(\omega)} |Z|_0^2 / 2\omega Z_0$$

$$\Re\{Z(\omega)\} = \frac{Z(\omega) + Z^*(\omega)}{2} = \frac{Z_0}{2} \left(\frac{1 + \Gamma(\omega)}{1 - \Gamma(\omega)} + \frac{1 + \Gamma^*(\omega)}{1 - \Gamma^*(\omega)} \right)$$

$$|Z_0 + Z(\omega)|^2 = Z_0^2 \left| \frac{1 + \Gamma}{1 - \Gamma} \right|^2 = \frac{Z_0^2}{2} \frac{(1 + \Gamma)^2 + (1 + \Gamma^*)^2}{(1 - \Gamma)(1 - \Gamma^*)}$$

$$= Z_0^2 \left| \frac{2}{1 - \Gamma} \right|^2 = \frac{4Z_0^2}{(1 - \Gamma)^2}$$

Think about this

$$\therefore IL = \frac{P_{av}}{P_L} = \frac{|V|^2 / 4Z_0}{\frac{4Z_0}{(1 - \Gamma)^2} Z_0} = \frac{1}{1 - \Gamma^2}$$

even function: define $|\Gamma(\omega)|^2 = \frac{M(\omega)^2}{N(\omega)^2}$

real polynomials

$$\therefore IL = \frac{1}{1 - \frac{M}{N}} = 1 + \frac{M}{N}$$

To design a filter, choose M and N to specify desired IL characteristics (Probs 8.3)

Procedure:


(1) Choose polynomial.

↳ LPF prototypes

(1) Maximally flat LPF :

$$IL = 1 + K^2 \left(\frac{\omega}{\omega_c} \right)^{2N}$$


filter order
cut-off freq.

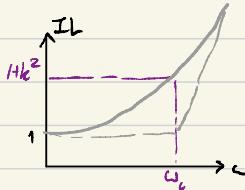

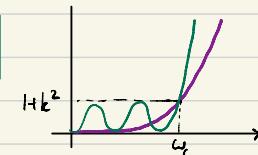(2) Equal ripple LPF

↳ Chebyshev polynomials (constant phase)

$$IL = 1 + K^2 T_N^2 \left(\frac{\omega}{\omega_c} \right)^2$$



(3) Other ...

(2) Convert polynomials into circuit. (Using lossless LC prototypes)

$$\begin{array}{ccccccccc} b_0 = S_0 = 1 & b_1 = g_2 & b_2 = g_3 & b_3 = g_4 & \dots & \sum b_n = 1 \\ \text{LC LPF prototype} & & & & & & & & \end{array}$$

(ex) 2nd-order maximally flat filter

$$IL = 1 + 1 \times \left(\frac{\omega}{\omega_c} \right)^{2N} = 1 + \left(\frac{\omega}{\omega_c} \right)^4$$

$$\begin{aligned} R &= 1 & L &= \frac{1}{j\omega_c} & \Sigma_{in} &= j\omega L + r \parallel \frac{1}{j\omega C} \\ & & & & &= j\omega L + r \frac{(1 - j\omega C)^2}{1 + \omega^2 C^2} \end{aligned}$$

$$IL = \frac{1}{1 - \Gamma^2} = \frac{1}{1 - \Gamma^4} = \frac{1}{1 - \frac{z-1}{z+1} \cdot \frac{(z-1)^2}{(z+1)^2}} = \frac{1}{2(z+1)}$$

$$z+2^{\frac{R}{L}} = \frac{2R}{1 + L^2 R^2 C^2}, z+1 = \dots$$

Eventually,

$$IL = 1 + \frac{1}{4R} \left[(1 - R^2) + (R^2 + L^2 - 2LCR^2) \omega^2 + L^2 C^2 R^2 \omega^4 \right]$$

→ to get $IL = 1 + \omega^4$

$$(1): 1 + \frac{1}{4R} (1 - R^2) = 1 \rightarrow R = 1$$


$$(2): \frac{1}{4R} (R^2 + L^2 - 2LCR^2) = 0 \rightarrow L = C \quad \left. \begin{array}{l} L = C = \frac{1}{\sqrt{2}} \end{array} \right\}$$

$$(3): \frac{1}{4R} L^2 C^2 R^2 = 1 \rightarrow LC = 2$$

(3) Scale filter prototype: scale of Z_0 and ω_c

Example LPF: $S_c = 2\text{GHz}$, 50Ω system, 15dB IL @ 3GHz

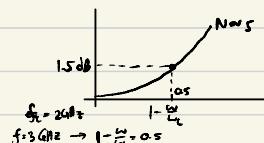(1) Find equation: maximally flat $IL = 1 + \left(\frac{\omega}{\omega_c} \right)^{2N}$




$N=5 \rightarrow$ Look at the table for $N=5$ (maximally flat)



$$C_n' = \frac{C_n}{\omega_c R_0} \neq$$

$$L_n' = \frac{R_0 L_n}{\omega_c}$$


② Filter transformation:

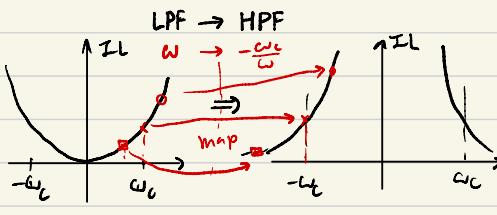

Apr 2

$$\text{series } \frac{g_k}{z_k} = j\omega g_k \text{ inductor} \rightarrow -jZ_0 \frac{L}{\omega} g_k \text{ capacitor}$$
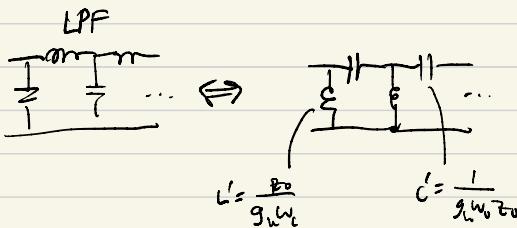
$$\text{shunt } \frac{y_k}{g_k} = j\omega g_k Y_0 \rightarrow -jY_0 \left(\frac{\omega}{\omega_0}\right) g_k \text{ inductor}$$



LPF → BSF





$$\omega \rightarrow \Delta \left(\frac{y_{in}}{y_{out}} - \frac{w_0}{\omega} \right)^{-1}$$

Filter implementation with distributed element


Recall

$$Z_{sc} = jZ_0 \tan \beta l \rightarrow \sim j\omega L' \text{ (inductor)}$$

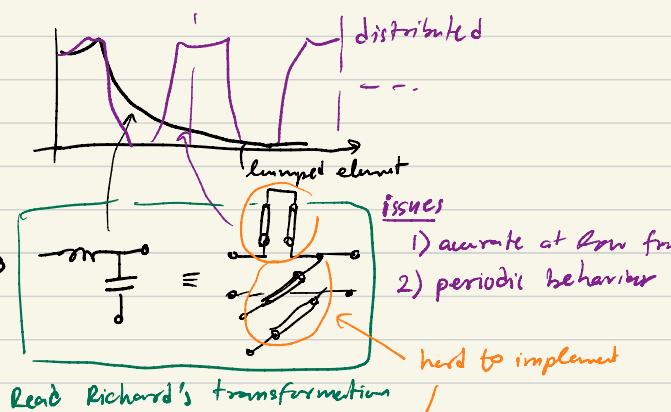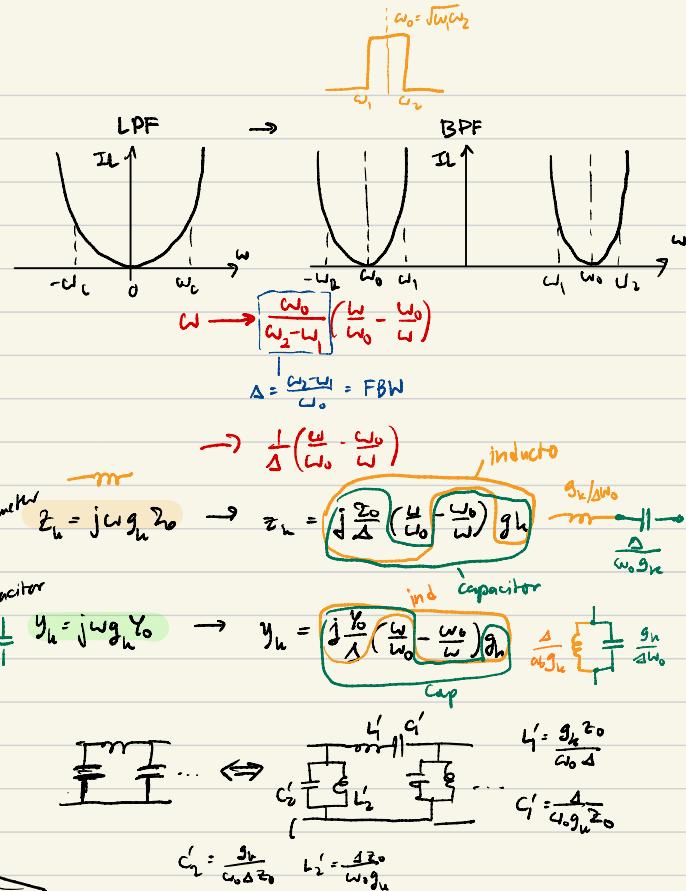
$$Y_{oc} = jY_0 \tan \beta l \rightarrow \sim j\omega C' \text{ (capacitor)}$$




Stepped impedance: (Pozar 8.6) - LPF

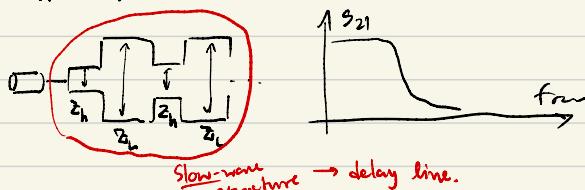

Coupled-line filter (BPF)

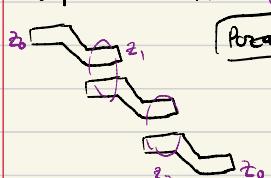

Coupled resonator filter.

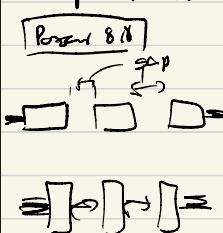

Kuroda's transform