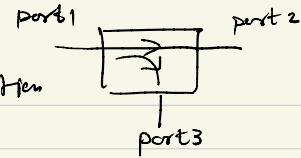


3 or 4 or more ports element.
they may have equal or unequal power distribution



Power Divider & Directional Coupler [Chap 7]

→ Three-port network

$$\begin{bmatrix} S_{11} & S_{12} & S_{13} \\ S_{21} & S_{22} & S_{23} \\ S_{31} & S_{32} & S_{33} \end{bmatrix}$$

• Possible property:

- ① Matched system: $S_{11} = S_{22} = S_{33} = 0$
- ② lossless $S^H S = I$
- ③ Reciprocal: $S^T = S$

It is impossible to construct a lossless reciprocal time-invariant 3-port system that is matched at every port.

Apr 7

Matched & Reciprocal network:

$$S = \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} \rightarrow S^H = \begin{bmatrix} 0 & S_{12}^H & S_{13}^H \\ S_{12}^H & 0 & S_{23}^H \\ S_{13}^H & S_{23}^H & 0 \end{bmatrix} \rightarrow \begin{bmatrix} 0 & S_{12}^H & S_{13}^H \\ S_{12}^H & 0 & S_{23}^H \\ S_{13}^H & S_{23}^H & 0 \end{bmatrix} \begin{bmatrix} 0 & S_{12} & S_{13} \\ S_{12} & 0 & S_{23} \\ S_{13} & S_{23} & 0 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \end{bmatrix} \rightarrow \text{To be lossless}$$

$$\text{Diag: } |S_{12}|^2 + |S_{13}|^2 = 1$$

$$|S_{12}|^2 + |S_{23}|^2 = 1$$

$$|S_{13}|^2 + |S_{23}|^2 = 1$$


$$S_{13}^H S_{23} = 0$$

$$S_{23}^H S_{12} = 0$$

$$S_{12}^H S_{13} = 0$$

(S_{13}, S_{23}, S_{12}) need at least two zeros, which will violate diagonal product condition.

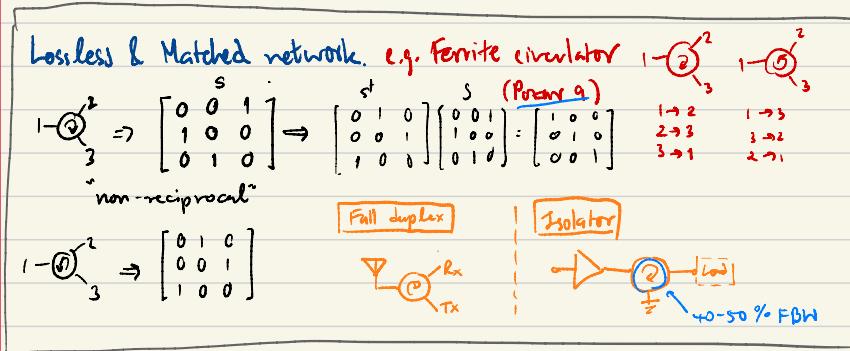∴ Matched & Reciprocal 3-port network cannot be lossless.



Matched, lossy, reciprocal. (resistor divider)


$$\begin{aligned} Z_{ii} &= \frac{Z_{in}}{Z_{in} + Z_i}, \quad Z_{in}^i = R_i + (R_j + Z_j) \parallel (R_k + Z_k) \\ &\text{Assume } Z_i = Z_j = Z_k = Z_0 \text{ and } R_i = R_j = R_k = R_0 \\ &\text{we get } S = \begin{bmatrix} 0 & V_2 & V_2 \\ \frac{1}{2} & 0 & \frac{1}{2} \\ \frac{1}{2} & \frac{1}{2} & 0 \end{bmatrix} \rightarrow \text{lossy, equally split power.} \end{aligned}$$

For incident on port 1
a, b could have the same potential, suggesting no current flow through R .

Wilkinson Power Divider (Pozar 7.3)

- ↳ Matched at all 3-ports,
- ↳ Good isolation between ports

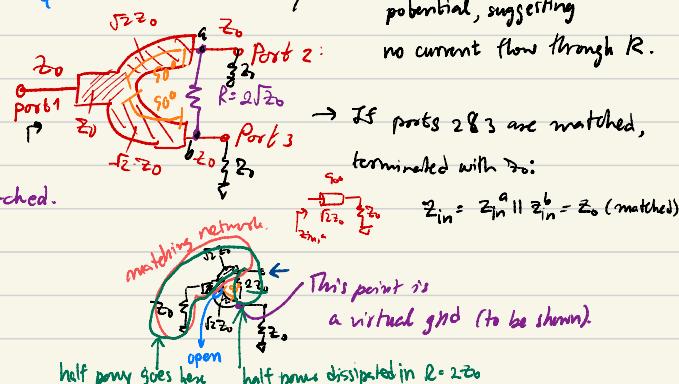- ↳ Lossy network but lossless when the output ports are matched.
Reflected power is dissipated.




$\frac{1}{2}$ -parameter of Wilkinson divider.

$$\begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ j/\sqrt{2} & 0 & 0 \\ -j/\sqrt{2} & 0 & 0 \end{bmatrix} \xrightarrow{\text{isolation}} \text{matched} \Rightarrow -\frac{j}{\sqrt{2}} \begin{bmatrix} 0 & 1 & 1 \\ 1 & 0 & 0 \\ 1 & 0 & 0 \end{bmatrix}$$

Even-odd mode analysis (symmetrically analyze)

↳ Many couplers exhibit high level of symmetry

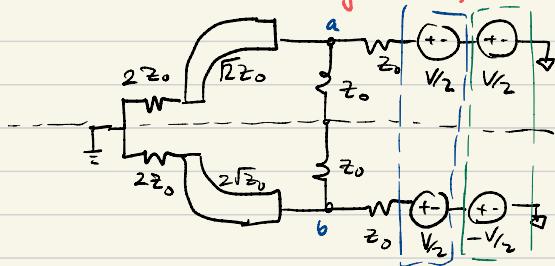⇒ can be analyzed using odd-even mode analysis.



Excitation at port 2 → even sources at ports 2 & 3 / separately analyze them
+ odd sources ————— and then superposition.

① Even-mode analysis:

→ Points a and b are at the same potential → no current → sym plane is "open"

$$R_L = \frac{(\sqrt{2}Z_0)^2}{2Z_0} = Z_0 \rightarrow \text{"matched"} \rightarrow \text{no scattering at ports 2 & 3}$$

in even mode.


$$V_2^{\text{even}} = V_3^{\text{even}} = \frac{V_0}{2} \cdot \frac{Z_0}{Z_0 + Z_0} = \frac{V_0}{4}$$

$$V_1^{\text{even}} = V^+ e^{j\theta(1-R_L)} = V^+ (1+R_L e^{j\theta}) e^{-j\theta} = V^+ (1-R_L) \quad \left| \frac{V_1^{\text{even}}}{V_2^{\text{even}}} = \frac{e^{j\theta(1-R_L)}}{1-R_L} = (-j) \frac{1+R_L}{1-R_L} = -j \frac{4}{2+R_L} \right.$$

$$\therefore V_1^{\text{even}} = -j \frac{4}{2+R_L} \cdot \frac{V_0}{4} = -j \frac{\sqrt{2}}{4} V_0$$

Apr 10 :

② Odd-mode analysis

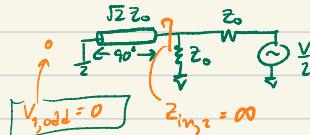

Port 2 (& 3) are matched

→ no scattering wave for odd mode.

$$V_1^{\text{odd}} = 0, \quad V_2^{\text{odd}} = \frac{V_0}{2} \cdot \frac{Z_0}{Z_0 + Z_0} = \frac{V_0}{4}, \quad V_3^{\text{odd}} = -V_2^{\text{odd}} = -\frac{V_0}{4}$$

Linear system: superposition

$$V_2 = V_2^{\text{even}} + V_2^{\text{odd}} = V_1 + V_3 = \frac{V_0}{2} \rightarrow \text{Matched input} \Rightarrow S_{22} = 0$$


$$V_3 = V_3^{\text{even}} + V_3^{\text{odd}} = V_1 + (-\frac{V_0}{4}) = 0 \rightarrow S_{32} = 0$$

$$V_1 = V_1^{\text{even}} + V_1^{\text{odd}} = -j \frac{\sqrt{2}}{4} V + 0 = -j \frac{\sqrt{2}}{4} V \rightarrow S_{12} = \frac{V_1^-}{V_2^+} = \frac{V_1^-}{V_2} (1+Z_{22}) = -j \frac{1}{\sqrt{2}}$$

$$\frac{Z_0}{Z_0 + Z_0} \frac{Z_0}{Z_0 + Z_0} G V$$

$$\left. \begin{array}{l} \therefore \text{symmetry: } \\ \begin{bmatrix} 0 & -j/\sqrt{2} & -j/\sqrt{2} \\ -j/\sqrt{2} & 0 & 0 \\ -j/\sqrt{2} & 0 & 0 \end{bmatrix} \end{array} \right\}$$

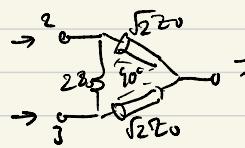We can use Wilkinson divider
as a combiner.




$$b_1 = -j/\sqrt{2} (a_2 + a_3)$$

$$\text{if } a_2 = a_3 = a \Rightarrow b_1 = -j\sqrt{2}a$$

$$|b_1|^2 = 2(a_1)^2$$


Branchline Coupler (Pozar 7.5)

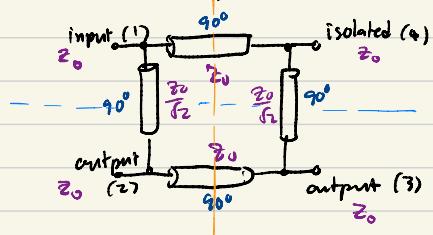

$$[S] = \frac{1}{\sqrt{2}} \begin{bmatrix} 0 & j & 1 & 0 \\ j & 0 & 0 & 1 \\ 1 & 0 & 0 & j \\ 0 & 1 & j & 0 \end{bmatrix}$$

Analysis of symmetric coupler using even-odd mode analysis

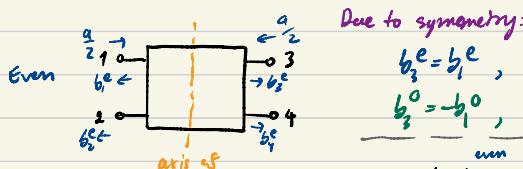Consider excitation at port 1 as superposition of even and odd mode excitation.




Due to symmetry:

$$b_3^e = b_1^e, \quad b_2^e = b_4^e$$

$$b_3^o = -b_1^o, \quad b_2^o = -b_4^o$$

even odd

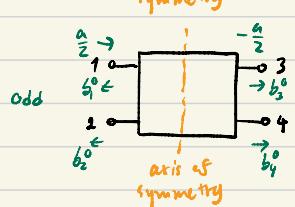

$$V_1^+ = \frac{a}{2} \sqrt{Z_0} + \frac{a}{2} \sqrt{Z_0} = a \sqrt{Z_0}$$

$$V_3^+ = \frac{a}{2} \sqrt{Z_0} - \frac{a}{2} \sqrt{Z_0} = 0$$

$$V_1^- = (b_1^e + b_1^o) \sqrt{Z_0}$$

$$V_2^- = (b_2^e + b_2^o) \sqrt{Z_0}$$

$$V_3^- = (b_3^e + b_3^o) \sqrt{Z_0} = (b_1^e - b_1^o) \sqrt{Z_0}$$

$$V_4^- = (b_4^e + b_4^o) \sqrt{Z_0} = (b_2^e - b_2^o) \sqrt{Z_0}$$

$$S_{11} = \frac{V_1^-}{V_1^+} = \frac{(b_1^e + b_1^o) \sqrt{Z_0}}{a \sqrt{Z_0}} = \frac{b_1^e + b_1^o}{a} = \frac{1}{2} \left(\frac{b_1^e}{a/2} + \frac{b_1^o}{a/2} \right) = \frac{1}{2} (S_{11}^e + S_{11}^o)$$

$$\therefore S_{11} = \frac{1}{2} (S_{11}^e + S_{11}^o)$$

$$S_{21} = \frac{V_2^-}{V_1^+} = \frac{(b_2^e + b_2^o) \sqrt{Z_0}}{a \sqrt{Z_0}} = \frac{b_2^e + b_2^o}{a} = \frac{1}{2} (S_{21}^e + S_{21}^o) \Rightarrow S_{21} = \frac{1}{2} (S_{21}^e + S_{21}^o)$$



$$S_{31} = \frac{V_3^-}{V_1^+} = \frac{(b_3^e + b_3^o) \sqrt{Z_0}}{a \sqrt{Z_0}} = \frac{b_3^e + b_3^o}{a} = \frac{1}{2} (S_{31}^e - S_{31}^o) \Rightarrow S_{31} = \frac{1}{2} (S_{31}^e - S_{31}^o)$$

$$S_{41} = \frac{V_4^-}{V_1^+} = \frac{(b_4^e - b_4^o) \sqrt{Z_0}}{a \sqrt{Z_0}} = \frac{b_4^e - b_4^o}{a} = \frac{1}{2} (S_{41}^e - S_{41}^o) \Rightarrow S_{41} = \frac{1}{2} (S_{41}^e - S_{41}^o)$$


Branchline coupler analysis

Branchline coupler has two-fold symmetry:

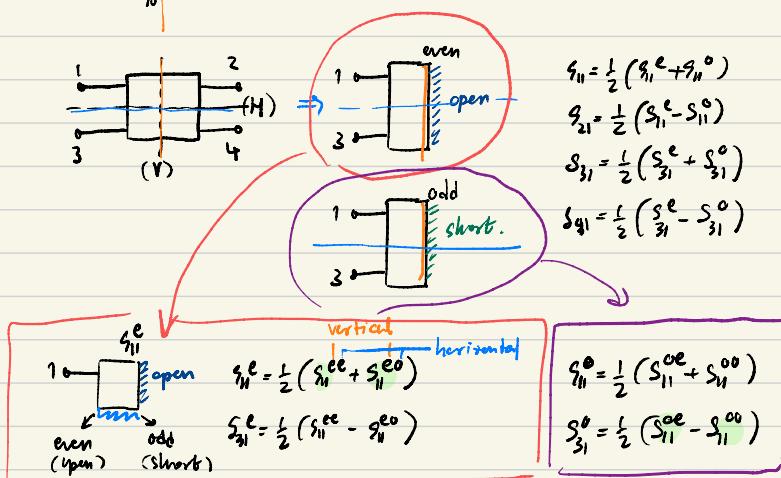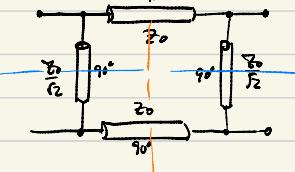→ Break the circuit twice using even-odd analysis.




1) Even-even mode

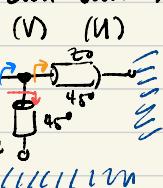

$$(V) \quad (H) \quad Z_{in}^1 = \frac{Z_0}{j \tan \theta} = \frac{Z_0}{j}, \quad Z_{in}^2 = \frac{Z_0 \sqrt{2}}{j} \rightarrow Z_{in}^{ee} = -j Z_0 || -j \frac{Z_0}{\sqrt{2}} = -j Z_0 \left(1 || \frac{1}{\sqrt{2}} \right) = -j Z_0 \frac{1}{1+\sqrt{2}}$$

$$\gamma_{11}^{ee} = \frac{Z_{in}^{ee} - Z_0}{Z_{in}^{ee} + Z_0} = \frac{-j \frac{1}{\sqrt{2}} - 1}{-j \frac{1}{\sqrt{2}} + 1} = \frac{\sqrt{2}}{2}(1-j)$$


2) Even-Odd mode

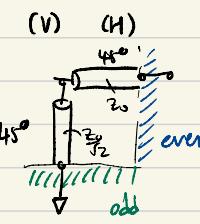

$$Z_{in}^{eo} = (-jZ_0) \parallel (j\frac{Z_0}{f_2}) \\ = jZ_0 (-1) \parallel \frac{1}{f_2} = jZ_0 \frac{1}{-1+f_2}$$

$$S_{11}^{eo} = \frac{Z_{in}^{eo} - Z_0}{Z_{in}^{eo} + Z_0} = \frac{jZ_0 - (f_2 - 1)Z_0}{jZ_0 + (f_2 + 1)Z_0} = \frac{f_2}{2}(j+1) = S_{11}^{ee}$$


3) Odd-even mode

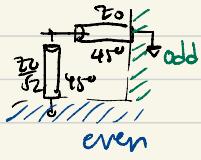

$$Z_{in}^{oe} = (jZ_0) \parallel (-j\frac{Z_0}{f_2}) \\ = jZ_0 (1) \parallel -\frac{1}{f_2} = jZ_0 \frac{1}{1-f_2}$$


$$\therefore S_{11}^{oe} = \frac{f_2}{2}(1-j) = S_{11}^{ee}$$

4) Odd-odd mode

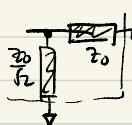

$$Z_{in}^{oo} = jZ_0 \parallel j\frac{Z_0}{f_2} = jZ_0 \frac{1}{1+f_2}$$
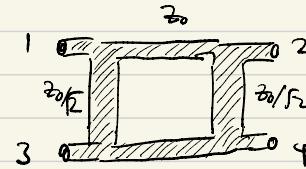
$$\therefore S_{11}^{oo} = \frac{f_2}{2}(-1+j) = -S_{11}^{ee}$$



$$S_{11}^e = \frac{1}{2}(S_{11}^{ee} + S_{11}^{eo}) =$$

$$S_{31}^e = \frac{1}{2}(S_{11}^{ee} - S_{11}^{eo}) =$$

$$S_{11}^o = \frac{1}{2}(S_{11}^{ee} + S_{11}^{oo}) =$$

$$S_{31}^o = \frac{1}{2}(S_{11}^{ee} - S_{11}^{oo}) =$$

$$S_{11} = \frac{1}{2}(S_{11}^e + S_{11}^o) = 0$$

$$S_{21} = \frac{1}{2}(S_{11}^e - S_{11}^o) = 0$$


$$S_{31} = \frac{1}{2}(S_{31}^e + S_{31}^o) = -\frac{j}{f_2}$$

$$S_{41} = \frac{1}{2}(S_{31}^e - S_{31}^o) = -\frac{1}{\sqrt{2}}$$

$$S = -\frac{1}{f_2} \begin{pmatrix} 0 & 0 & 0 & 0 \\ 0 & 0 & 1 & j \\ j & 1 & 0 & 0 \\ 1 & j & 0 & 0 \end{pmatrix}$$

90-deg hybrid coupler

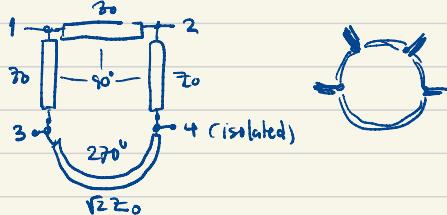
180° hybrid coupler → birefringent coupler (Pozar 7.8)



Coupler applications

$$\begin{matrix} 1 & 2 \\ 3 & 4 \end{matrix} \quad S = -\frac{1}{f_2} \begin{pmatrix} 0 & 0 & j & 1 \\ 0 & 0 & j & 1 \\ j & 1 & 0 & 0 \\ 1 & j & 0 & 0 \end{pmatrix}$$

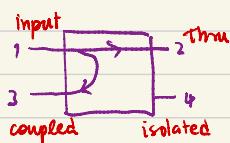Symbols and terminology for general 4-port coupler



Return Loss (RL) : $RL = -20 \log |S_{11}|$

Insertion Loss (IL) : $IL = -20 \log |S_{21}|$

Coupling (C) : $C = -20 \log |S_{31}|$

Directivity (D) : $D = 10 \log (P_3/P_4)$
 $= -20 \log |S_{41}/S_{31}|$

Couplers & Amplifiers

$$\begin{aligned} a_1 &\rightarrow \begin{pmatrix} b_2 \\ b_3 \end{pmatrix} & |S_{11}| = G_1 = \begin{pmatrix} b_1' \\ a_1' \end{pmatrix} \\ b_1 & \left(\begin{array}{cc} S_{11} & S_{12} \\ S_{21} & S_{22} \end{array} \right) & \xrightarrow{\text{amplifiers}} \begin{pmatrix} a_3' \\ b_3' \end{pmatrix} \xrightarrow{\text{90-deg}} \begin{pmatrix} a_2' \\ b_2' \end{pmatrix} \xrightarrow{\text{amplifiers}} \begin{pmatrix} a_4' \\ b_4' \end{pmatrix} \xrightarrow{\text{90-deg}} \begin{pmatrix} a_1' \\ b_1' \end{pmatrix} \\ a_1 & \xrightarrow{j/\sqrt{2}} b_2 & \xrightarrow{-1/\sqrt{2}} a_3' \\ b_1 & \xrightarrow{-1/\sqrt{2}} a_2' & \xrightarrow{-1/\sqrt{2}} b_4' \end{aligned}$$

• Reflection : $\frac{b_1'}{a_1'} = \left(\frac{-j}{\sqrt{2}}\right) R \left(\frac{-j}{\sqrt{2}}\right) + \left(-\frac{1}{\sqrt{2}}\right) R \left(\frac{-1}{\sqrt{2}}\right) = 0$

• Transmission : $\frac{b_4'}{a_1'} = \left(\frac{-j}{\sqrt{2}}\right) G \left(\frac{1}{\sqrt{2}}\right) + \left(\frac{-1}{\sqrt{2}}\right) G \left(\frac{-1}{\sqrt{2}}\right) = j S_{21}$


Get ① same power gain as a single amplifier

② provide match over the BW of hybrid coupler

③ enlarge power handling (split input power into two amplifiers)



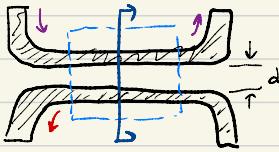Coupled transmission line coupler (Pozar 7.6)




Constructed from two TLs
with enough coupling E/M fields
→ tapped line?


Advantages i) Broadband

ii) Wide range of coupling (tuning the distance)

capacitive vs. inductive couplings

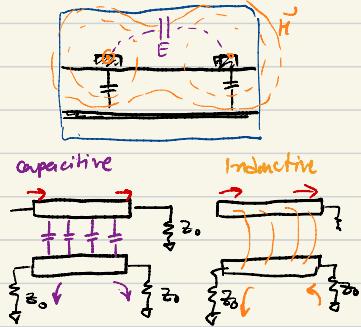


Even-Odd mode analysis

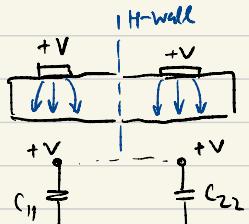

$$C_{ee} = C_{11} = C_{22}$$
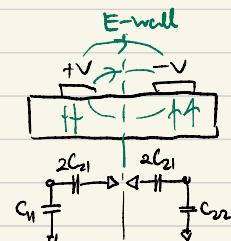
$$\sum_0^e = \sqrt{\frac{L_e}{C_{ee}}} = \sqrt{\frac{L_e C_e}{C_{ee}^2}} = \frac{1}{v_p C_e}$$







$$\therefore C_o^0 = C_{11} + 2C_{21}$$

$$\sum_0^o = \sqrt{\frac{L_o}{C_o^0}} = \sqrt{\frac{L_o C_o}{C_o^0 C_e}} = \frac{1}{v_p C_e}$$

$$\text{TEM waveguide } \rightarrow \text{same } v_p = \frac{1}{\sqrt{C_e}} = \frac{1}{\sqrt{C_o}}$$

Design of coupled line coupler

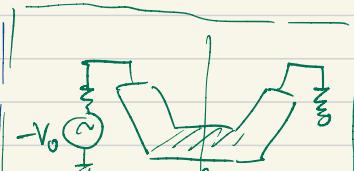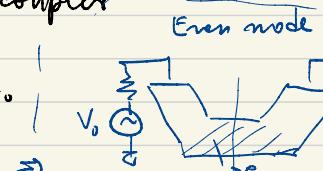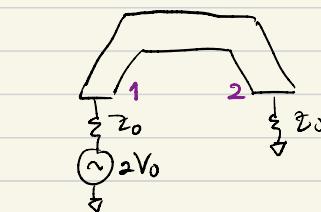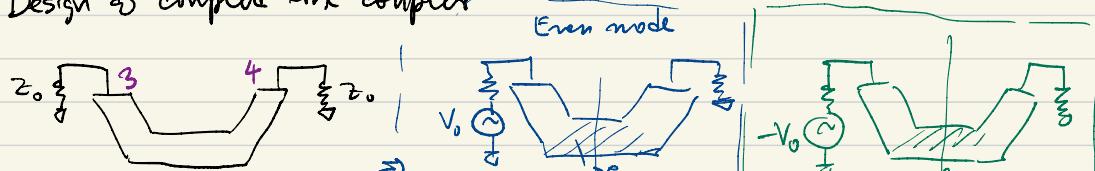

$$Z_{in}^e = Z_0 \frac{Z_0 + j Z_0 \tan \beta l}{Z_0 + j 2 Z_0 \tan \beta l}$$

$$V_1^e = V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0}$$

$$I_1^e = V_0 \frac{1}{Z_{in}^e + Z_0}$$

$$V_1^o = V_0 \frac{Z_{in}^o}{Z_{in}^o + Z_0}$$

$$I_1^o = V_0 \frac{1}{Z_{in}^o + Z_0}$$

$$Z_{in}^o = Z_0 + j \frac{Z_0 + j Z_0 \tan \beta l}{Z_0 + j 2 Z_0 \tan \beta l}$$

$$Z_{in} = \frac{V_1}{I_1} = \frac{V_1^e + V_1^o}{I_1^e + I_1^o} = \frac{V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0} + V_0 \frac{Z_{in}^o}{Z_{in}^o + Z_0}}{V_0 \frac{1}{Z_{in}^e + Z_0} + V_0 \frac{1}{Z_{in}^o + Z_0}} = Z_0 + \frac{2(Z_{in}^e Z_{in}^o - Z_0^2)}{Z_{in}^e Z_{in}^o + 2Z_0}$$

Apr 16

Matching condition $\Rightarrow Z_{in} = Z_0$


$$\therefore Z_0 = Z_{in}^e Z_{in}^o \quad ! \rightarrow \text{matching condition. (1)}$$

$$\text{let } Z_0 = \sqrt{Z_0^e Z_0^o},$$

$$Z_{in}^e = Z_0 \frac{\sqrt{Z_0^e} + j \sqrt{Z_0^o} \tan \beta l}{\sqrt{Z_0^e} + j \sqrt{Z_0^o} \tan \beta l}$$

$$Z_{in}^o = Z_0 \frac{\sqrt{Z_0^e} + j \sqrt{Z_0^o} \tan \beta l}{\sqrt{Z_0^e} + j \sqrt{Z_0^o} \tan \beta l}$$
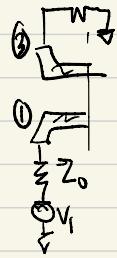
$$Z_{in}^e Z_{in}^o = Z_0^e Z_0^o = Z_0^2$$



Want to determine the coupling:

$$V_3 = V_3^0 + V_3^e = V_1^e - V_1^0 = V_0 \frac{Z_{in}^e}{Z_{in}^e + Z_0} - V_0 \frac{Z_{in}^0}{Z_{in}^0 + Z_0}$$

$$= V_0 \frac{j(Z_0^e - Z_0^0) \cdot \tan\theta}{2Z_0 + j(Z_0^e + Z_0^0) \tan\theta} = V_0 \frac{j(Z_0^e - Z_0^0)}{\frac{2Z_0}{\tan\theta} + j(Z_0^e + Z_0^0)}$$

$$V_3 = V_0 \frac{Z_0^e - Z_0^0}{Z_0^e + Z_0^0} = CV_0$$

if $\theta = 90^\circ$

Define as C : coupler factor

Super long calculation:

$$V_4 = V_4^e + V_4^0 = V_2^e - V_2^0 = 0$$

$$V_2 = V_2^e + V_2^0 = V_0 \frac{\sqrt{1-C^2}}{\sqrt{1-C^2} \cdot \cos\theta + j \sin\theta} = -jV_0 \sqrt{1-C^2}$$

$\theta \text{ if } \theta = \frac{\pi}{2}$


So far, we get

\star $Z_0^e = Z_0 \sqrt{\frac{1+C}{1-C}}$ \star $Z_0^0 = Z_0 \sqrt{\frac{1-C}{1+C}}$ \star (2)

Energy conservation.

Noise & Nonlinearity in Microwave System

• Dynamic Range & Sources of noise

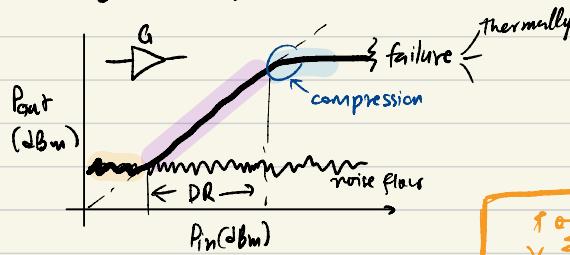


[Sources of noise]

- Thermal noise \rightarrow Johnson's \rightarrow Brownian motion
- Shot noise
- Generation-Recombination \rightarrow Quantum noise
- Polder ($1/f$)



Thermal noise

Noise power & Equivalent noise temp.

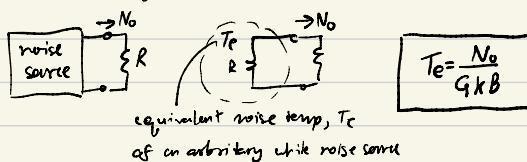


Rayleigh-Jeans approx.: $V_n = \sqrt{4kTBR}$

Resistance (Ω) , Bandwidth (Hz) , Temp (K)

How to measure T_e ?
 $\Rightarrow \gamma$ -method (Boyer 10)

\star

Noise figure : F

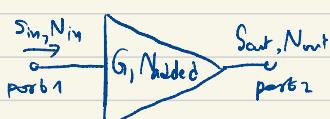

$$F = \frac{SNR_{out}}{SNR_{in}} = \frac{S_{out}N_{in}}{S_{in}N_{out}}$$

$S_{out} = G \cdot S_{in}$ amplified noise

$$N_{out} = G \cdot N_{in} + N_{added}$$

$$F = 1 + \frac{N_{added}}{G \cdot N_{in}}$$

Always > 1

System
need a definition, i.e., $R \otimes 290 K$

$$F = 1 + \frac{N_{added}}{G \cdot 4kTBR}$$